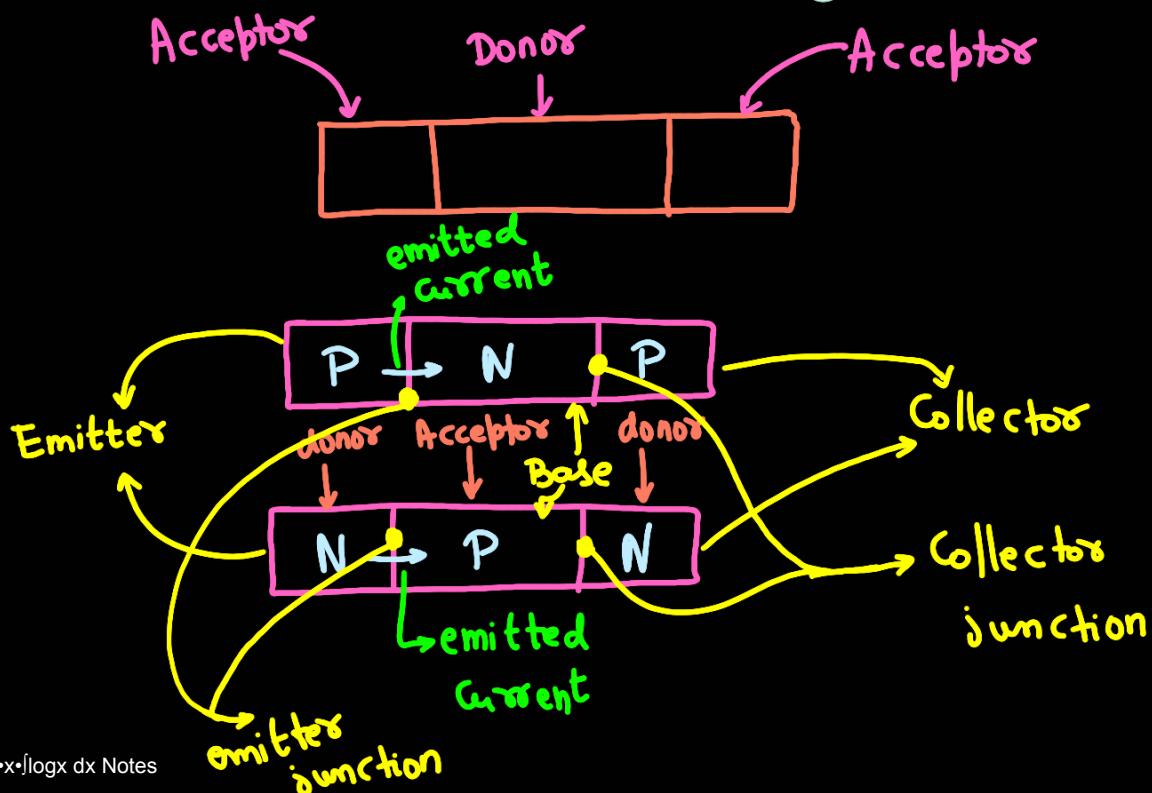


$$\text{Gain} = \frac{\text{O/P}}{\text{I/I P}}$$

### ★ Transistor


- Single crystal made of Si or Ge
- Crystal is continuous, such that 2 junctions are formed
- Can be either PNP or NPN



\* There are three regions in transistor :-

- ① Emitter :- Provides large numbers of charge carriers. Heavily doped and moderately sized
- ② Base :- Very thin & lightly doped
- ③ Collector :- Large in size & moderately doped

# Ckt symbol of transistor :-

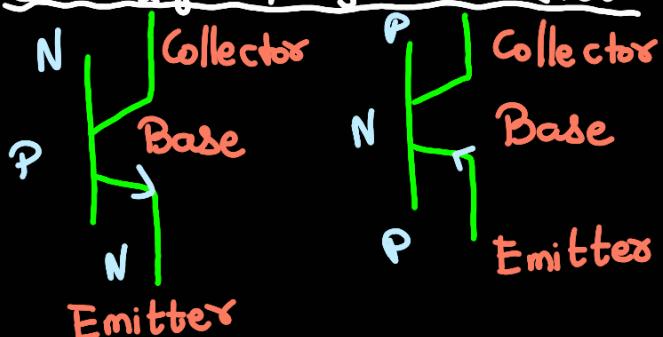

N-P-N  
transistor

P-N-P transistor

Note :  
Arrow always  
in dirn of  
forward  
Bias,  
i.e. from  
P to N


# Transistor Configurations :-

- ① Common Base (CB)
- ② Common Emitter (CE)
- ③ Common Collector (CC)

4 H Parameters:  
Input Impedance  
Reverse Voltage Ratio  
&  
Output Admittance  
Forward Current Gain

$\left. \begin{matrix} I/P \\ O/P \end{matrix} \right\}$

## # Common Base (CB) Configuration:-

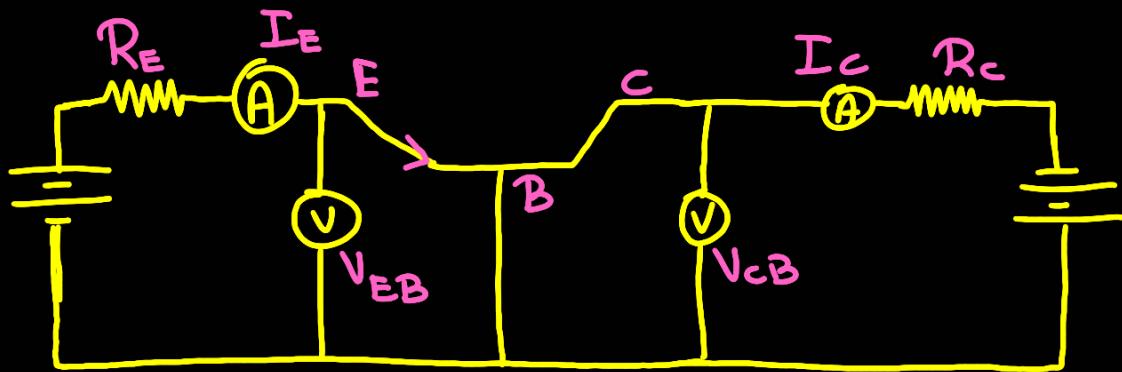


Input Circuit  
( $V_{EB}$ ,  $I_E$ )

Output Circuit  
( $V_{CB}$ ,  $I_C$ )

I/P characteristics

O/P characteristics



\* I/P characteristics:-

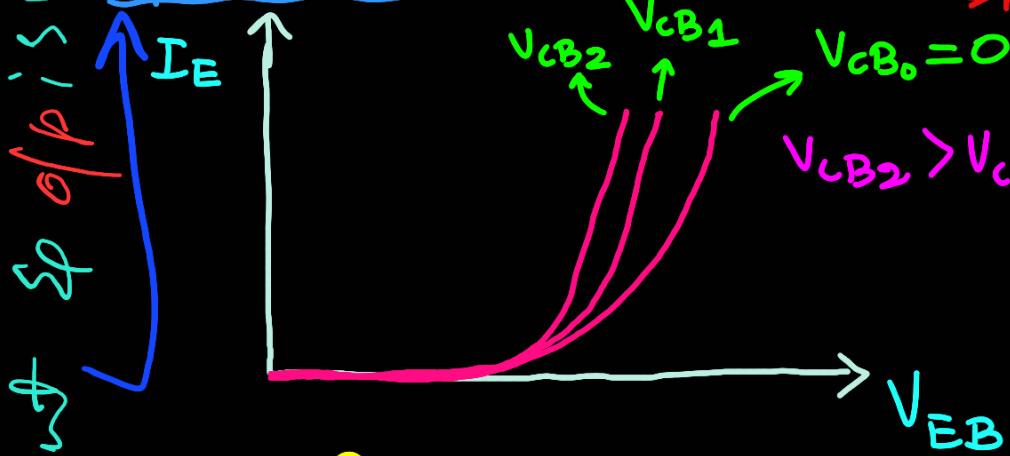

Always before  
 $V_{CB_0} = 0$   $V_{CB_0}!!!$

$V_{CB_2} > V_{CB_1} > V_{CB_0}$

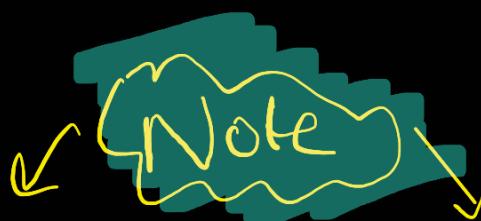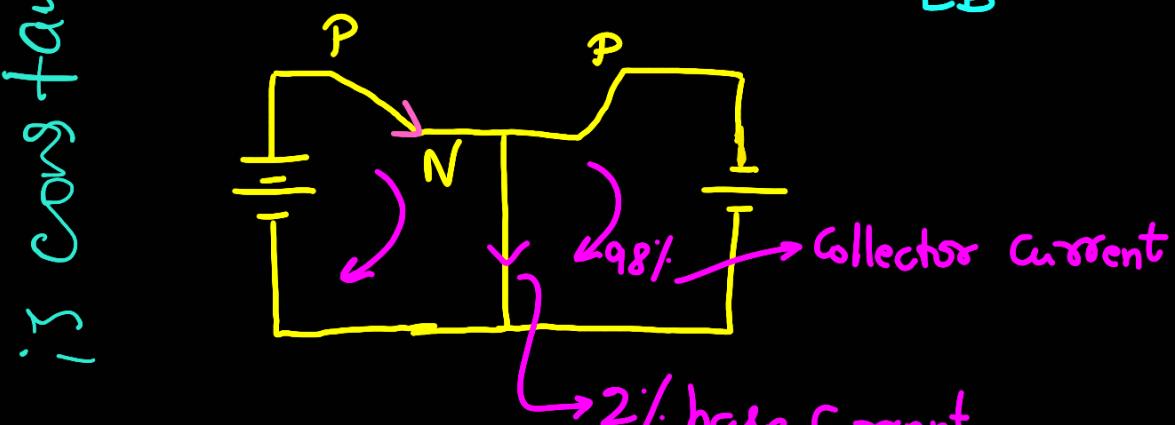input characteristics  
is constant & p of p



Emitter  $\delta^n \rightarrow$  F.B ; Collector  $\delta^n$  is reverse biased

I/P resistance

$$R_I = \frac{V_{EB}}{I_E} \quad \left|_{V_{CB}} \quad \delta_i = \frac{\Delta V_{EB}}{\Delta I_E} \right|_{V_{CB}}$$

Static


Dynamic

I/P  
resistance

I/P impedance
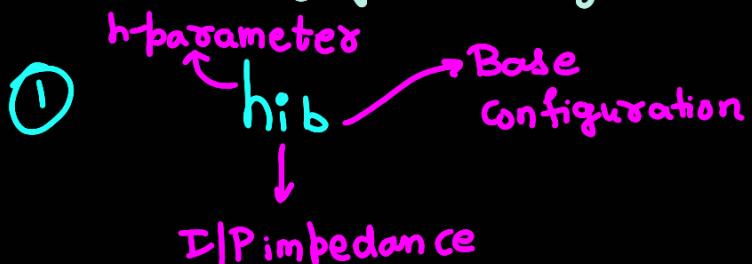
# h-parameters:-

↳ A way of measuring → alternative for ohm's law



$$h_{ib} = \frac{\Delta V_{EB}}{\Delta I_E} \quad \left|_{V_{CB}} \right.$$

② Reverse voltage ratio (h-parameters)



$h_{\sigma b}$   $\rightarrow$  Common base configuration  
reverse voltage ratio

$$\frac{O/P}{I/P}$$

But here  
∴ reverse ratio  
its  $\frac{I/P}{O/P}$

$$h_{\sigma b} = \frac{\Delta V_{EB}}{\Delta V_{CB}} \quad \left|_{I_E} \right.$$

## # Output characteristics:-

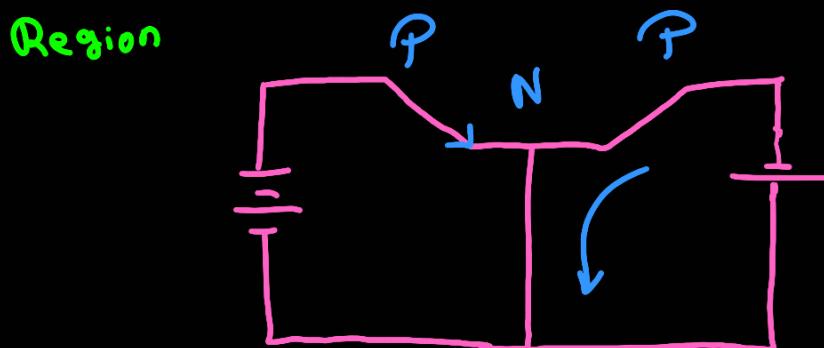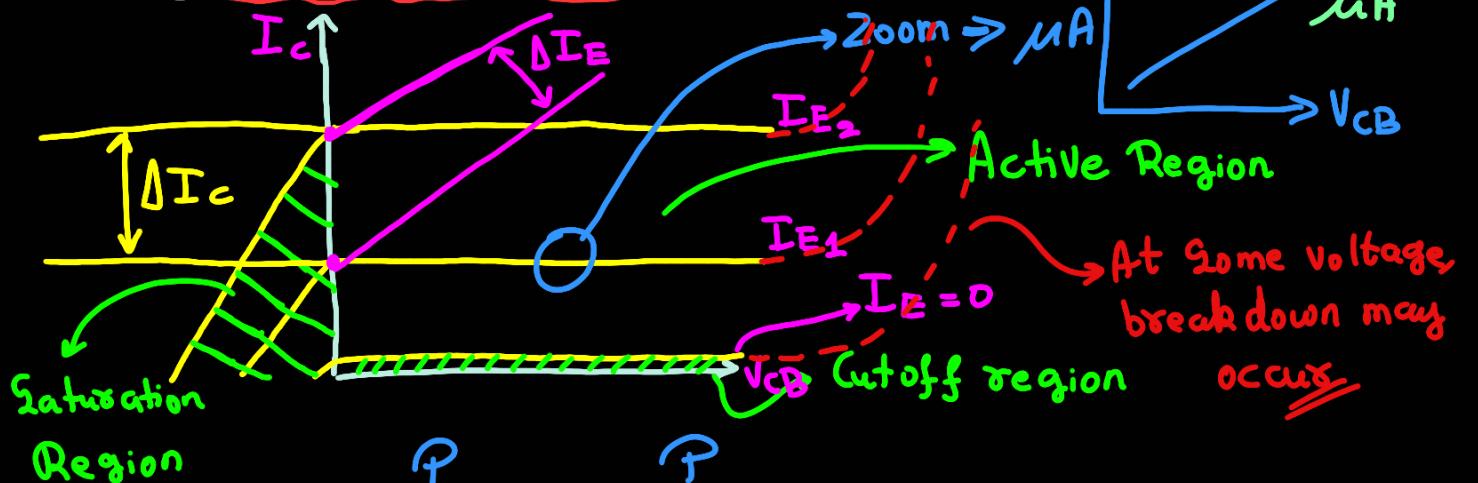

① O/P impedance

$$R_o = \left. \frac{V_{CB}}{I_c} \right|_{I_E}$$

①  $h_{ob} = \left. \frac{\Delta I_c}{\Delta V_{CB}} \right|_{I_E}$

O/P admittance      Common base configuration

In off char O/P is constant if f/p keeps on varying.

②  $h_{fb} = \left. \frac{\Delta I_c}{\Delta I_E} \right|_{V_{CB}} = \alpha \rightarrow AC$


forward current gain      Common Base config

Output current  
Input current

$$\alpha_{DC} = \frac{I_c}{I_D}$$

Output  
Input
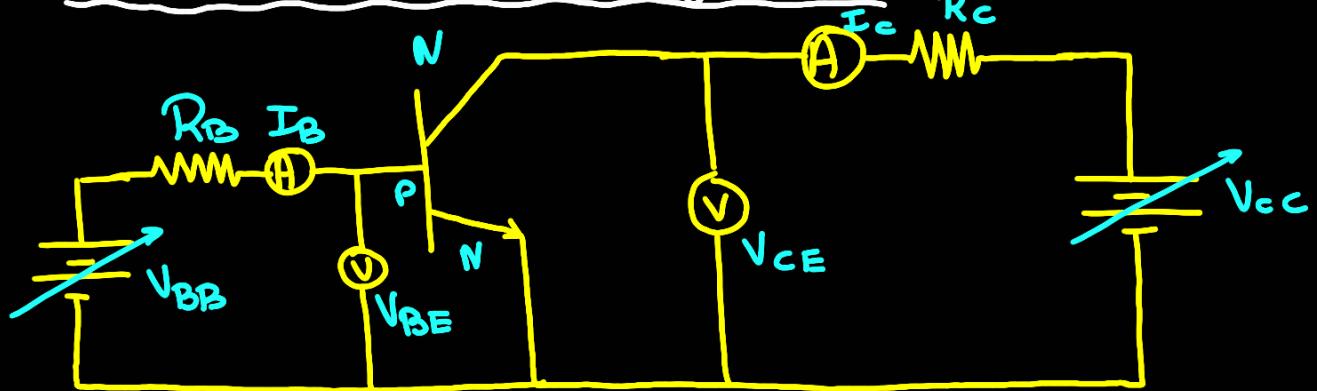
## # Common Emitter (CE) Configuration :-




I/P ckt  
( $V_{BE}$ ,  $I_B$ )

O/P ckt  
( $V_{CE}$ ,  $I_C$ )

Emitter jn is F.B  
Collector jn is R.B

★ Input Characteristics

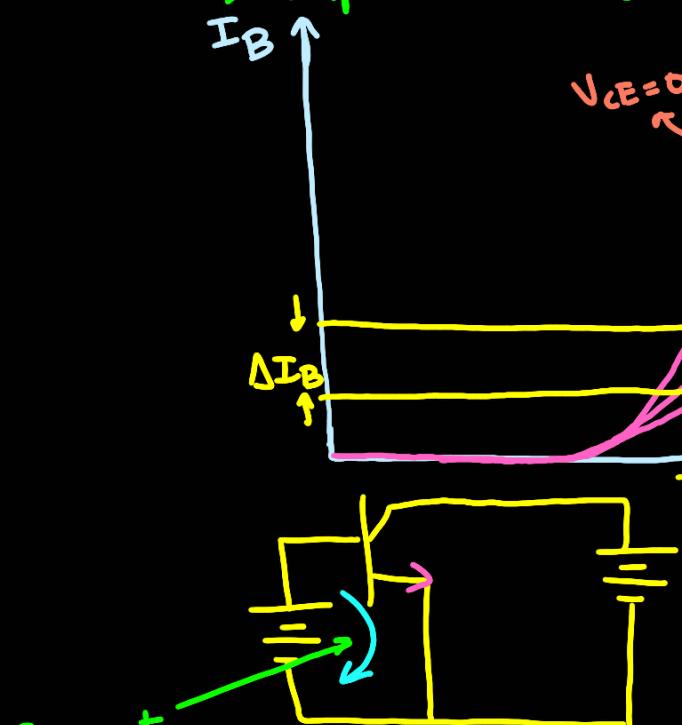

Current flow direction  
h-parameter

$$\textcircled{1} \quad h_{ie} = \frac{\Delta V_{BE}}{\Delta I_B} \Big|_{V_{CE}}$$

I/P impedance      (E config)



$$\textcircled{2} \quad h_{re} = \frac{\Delta V_{BE}}{\Delta V_{CE}} \Big|_{I_B}$$

reverse voltage ratio      (E config)

$V_{C2} > V_{C1} > V_{CE0}$

graph goes forward as O/P off ↑,  
(Unlike CB, whose graph goes backward)

## \* Output characteristics :-

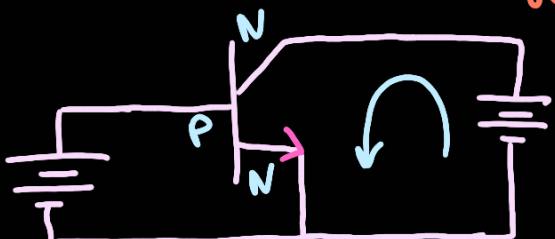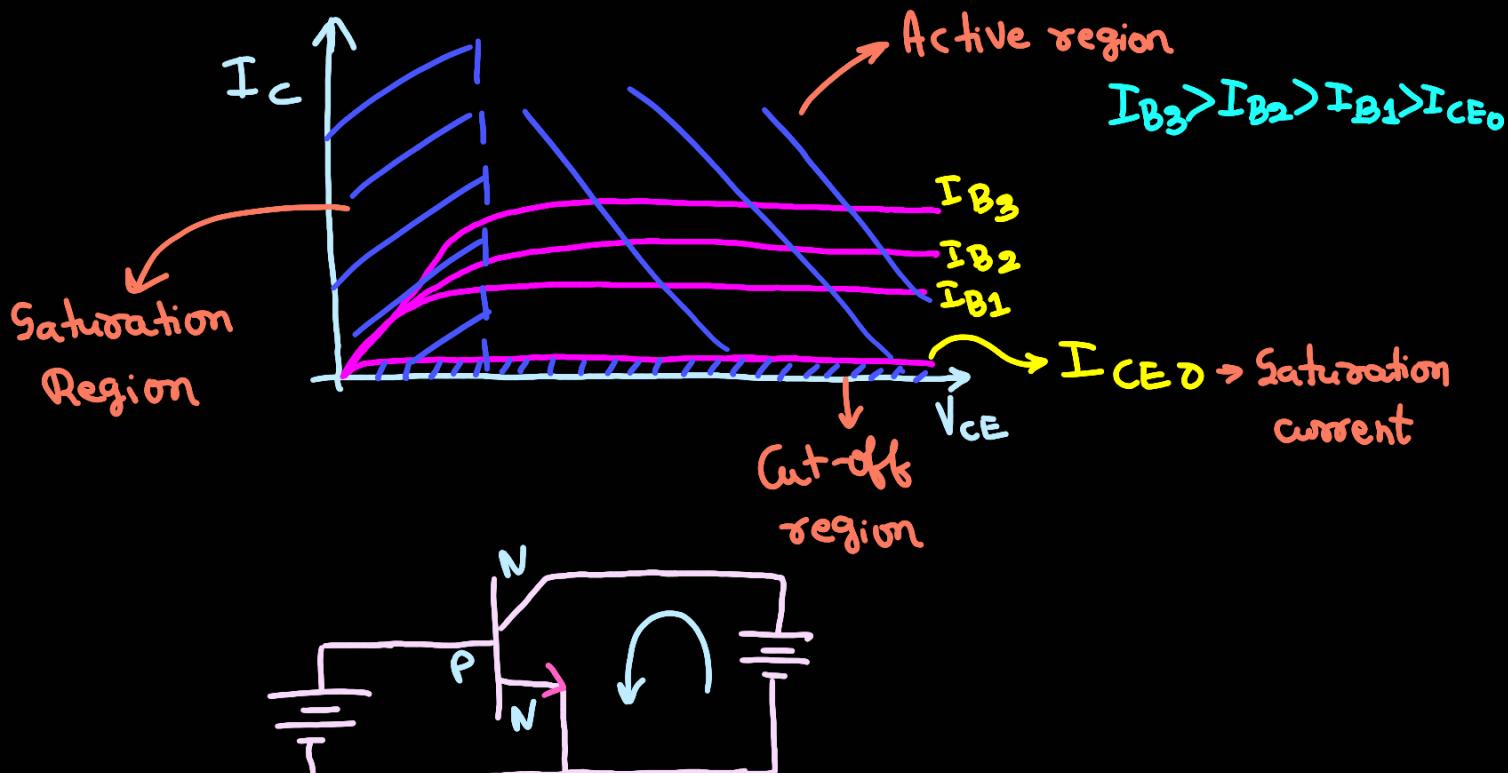

$$\textcircled{1} h_{oe} = \left. \frac{\Delta I_c}{\Delta V_{CE}} \right|_{I_B}$$

o/p admittance

$$\textcircled{2} h_{fe} = \left. \frac{\Delta I_c}{\Delta I_B} \right|_{V_{CE}} = \beta$$

forward current gain

## # Relation b/w $\alpha$ & $\beta$ :-

$$\text{W.K.T : } I_E = I_B + I_C \quad \text{throughout}$$

$$I_E = I_B + I_C$$



$$\frac{I_E}{I_C} = \frac{I_B}{I_C} + 1$$

$$\Rightarrow \frac{1}{\alpha} = \frac{1}{\beta} + 1$$

$$\alpha = \frac{I_C}{I_E} \quad \beta = \frac{I_C}{I_B}$$

Required relation

## # Common Collector Configuration :-

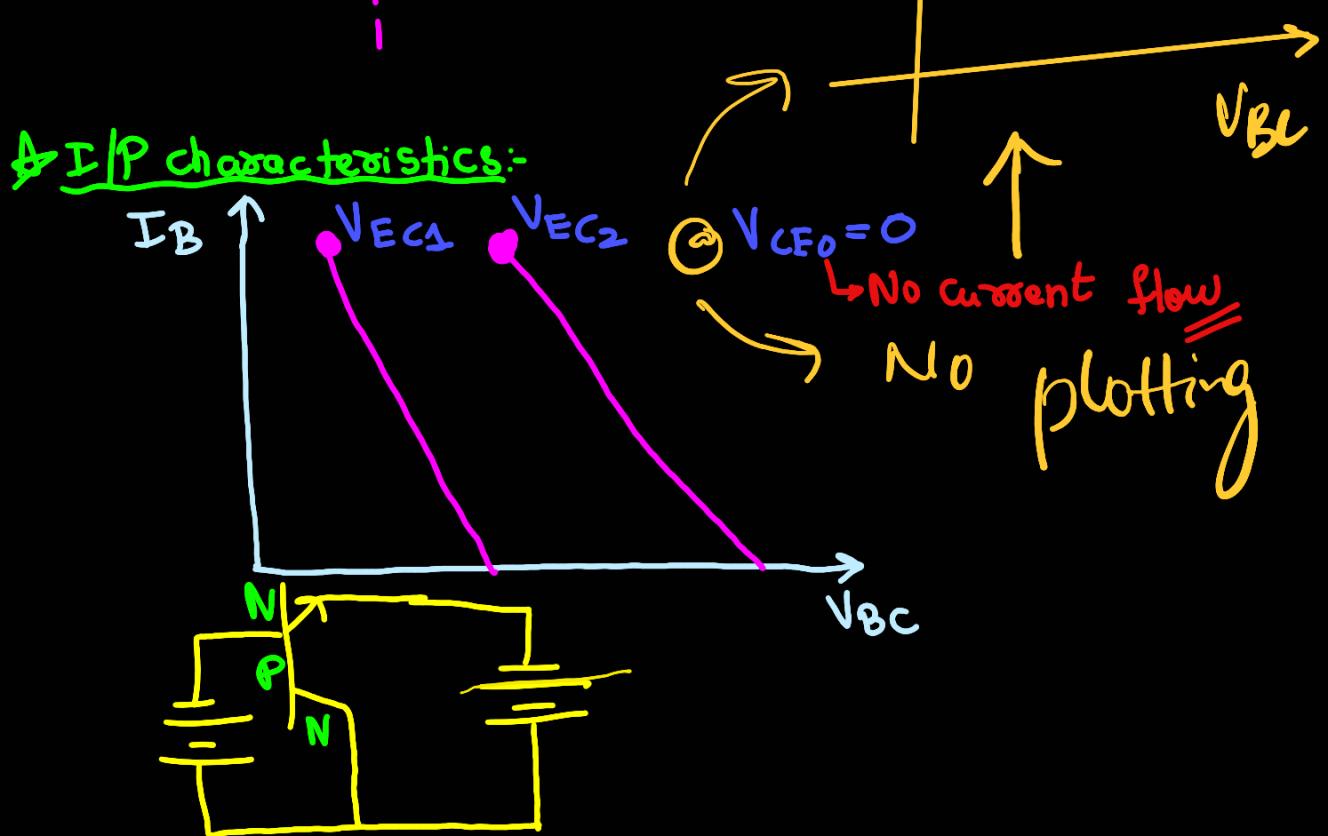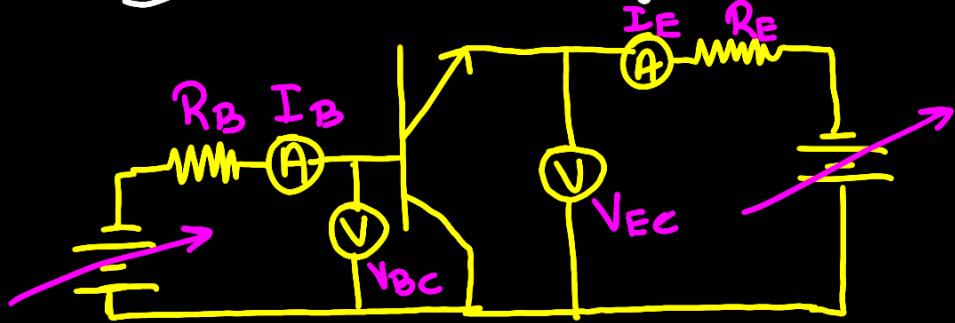


$$\textcircled{1} h_{ic} = \left. \frac{\Delta V_{Bc}}{\Delta I_B} \right|_{V_{EC}}$$

I/P impedance

$$\textcircled{2} h_{oc} = \left. \frac{\Delta V_{Bc}}{\Delta V_{EC}} \right|_{I_B}$$

Reverse voltage ratio

## \* O/P characteristics:-

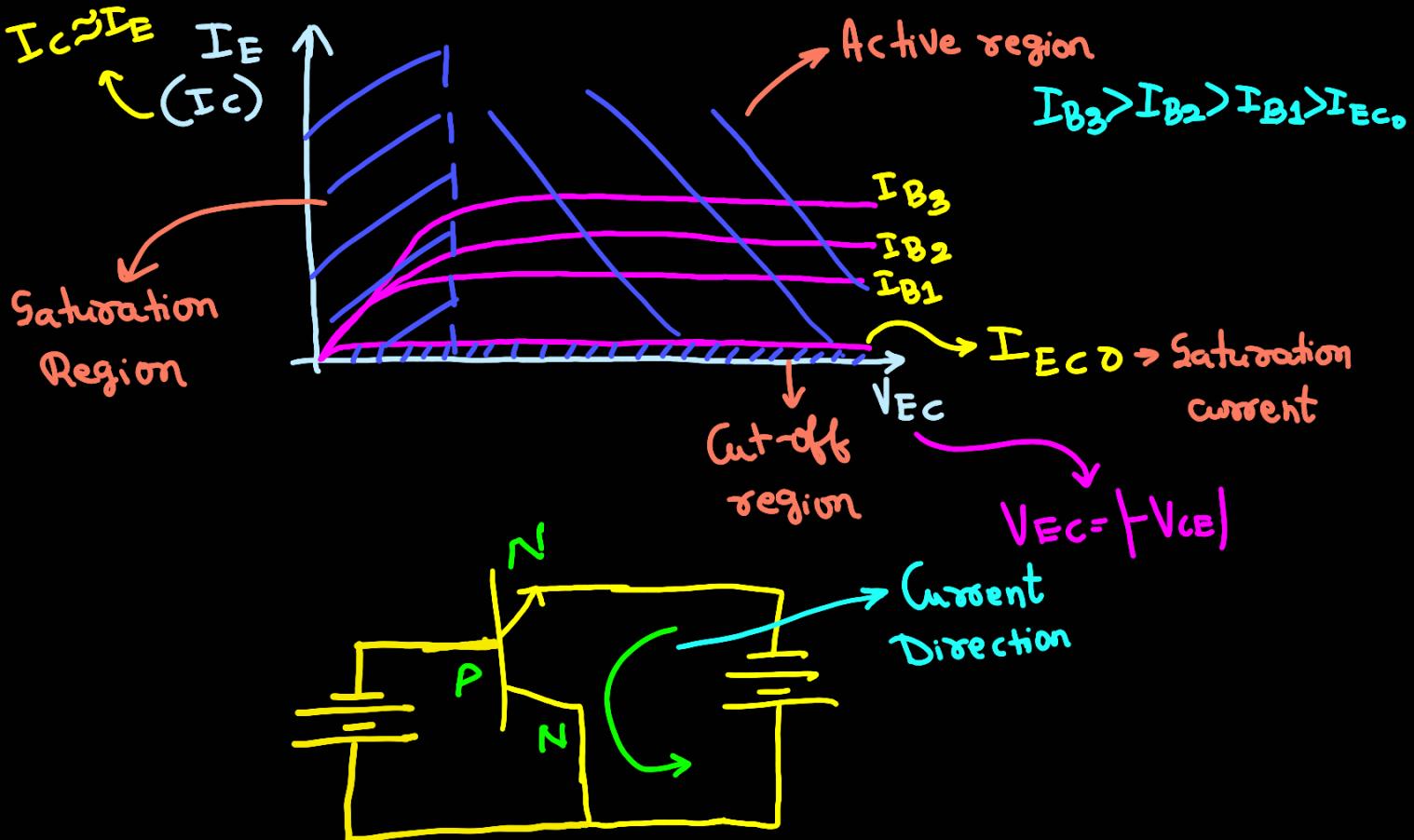

$$\textcircled{1} \quad h_{OC} = \left. \frac{\Delta I_E}{\Delta V_{EC}} \right|_{I_B}$$

O/P admittance

$$\textcircled{2} \quad h_{fC} = \left. \frac{\Delta I_E}{\Delta I_B} \right|_{V_{EC}} = \{$$

forward  
current gain

## # Relation b/w $\alpha$ , $\beta$ , $\gamma$ :



$$\{ = \beta + 1$$

$$\gamma = \frac{1}{1 - \alpha}$$

\*Derivation not  
necessary

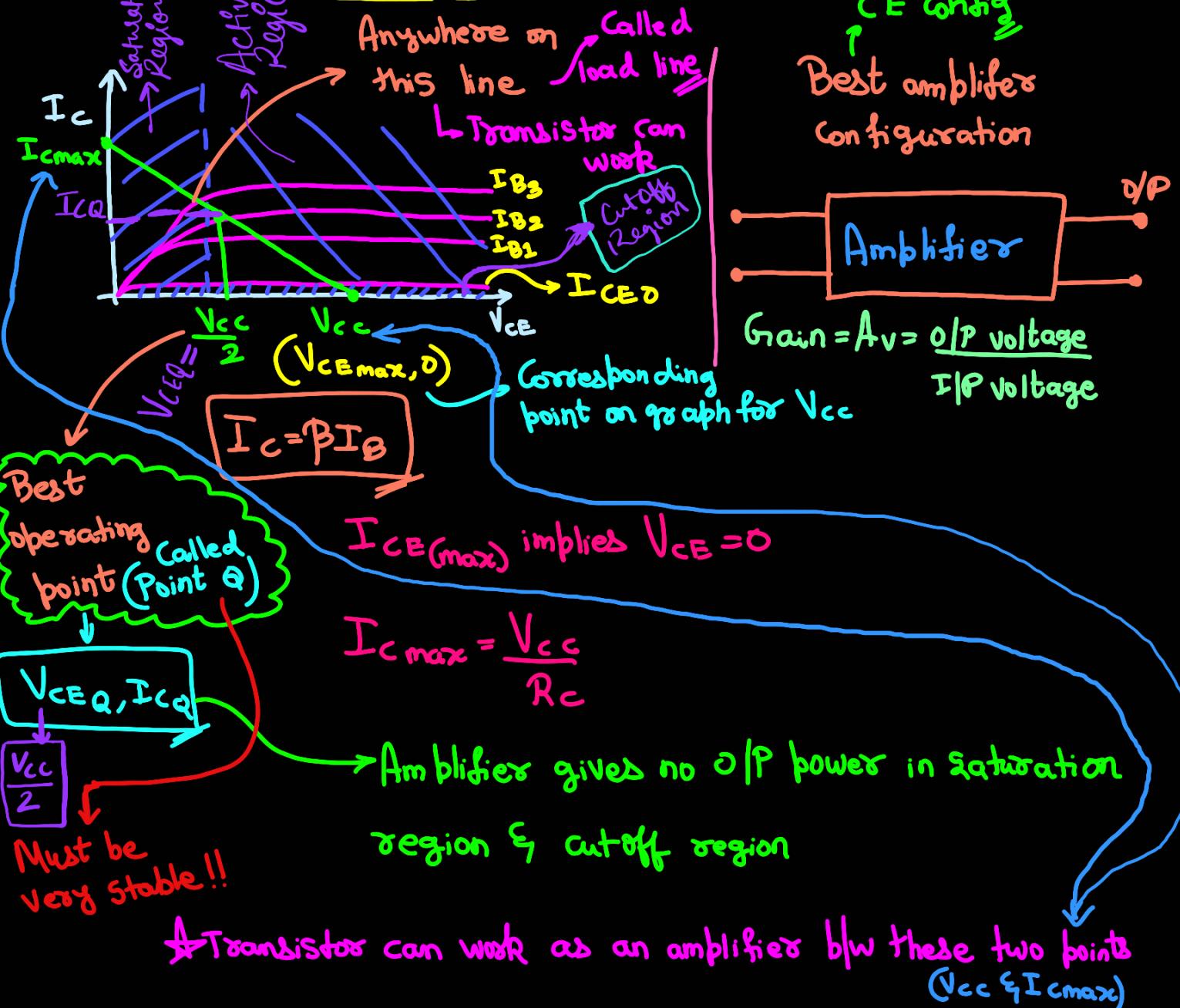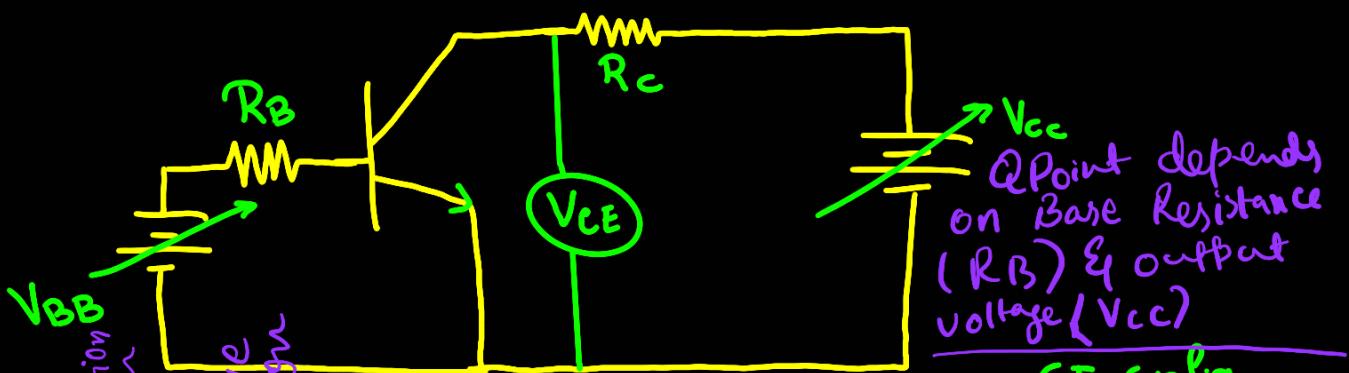
## # DC analysis:-

Consider CE Configuration & its O/P characteristics




★ Load Line:- Locus of the transistor operating points
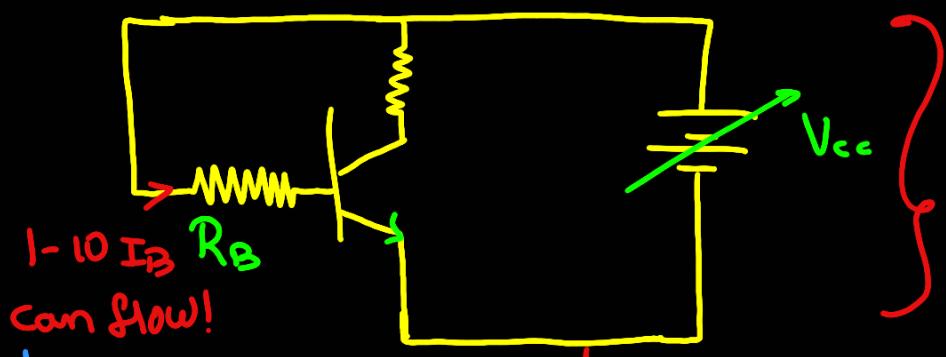
$$V_{CEQ} = \frac{V_{CC}}{2}; I_{CQ} = I_C$$




Due to ripple from rectifier O/P,  $I_B \& I_c$  can vary accordingly

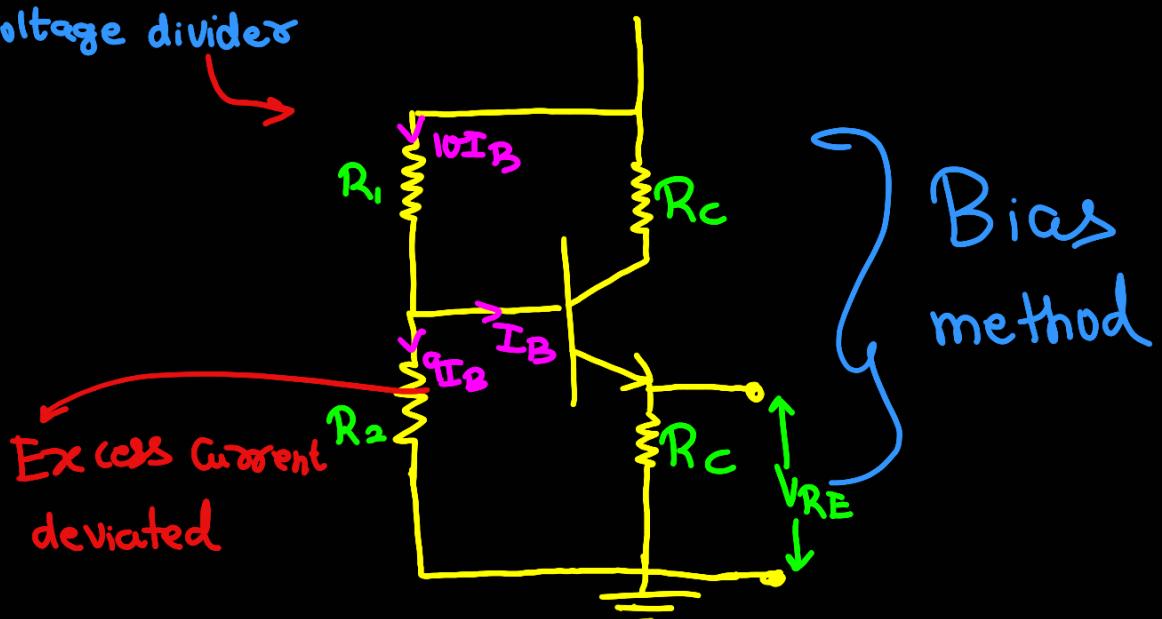To avoid  $\xi$ , maintain constant  $I_B$  in Base, add voltage dividers



Bias method

### Bias method:-

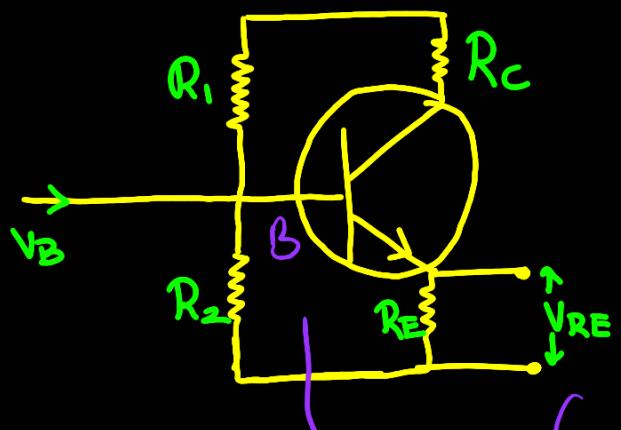


Common Emitter Configuration

$$R_B = \frac{R_1 + R_2}{R_1 R_2}$$

## Functions :-

- i)  $R_C$  :- Limit Collector current; Act as load resistor
- ii)  $R_1 \& R_2$  :- AC biasing resistors (Voltage divider bias)
- iii)  $R_E$  :- Emitter resistor used for stabilising Q point

## # RC coupled amplifier :-

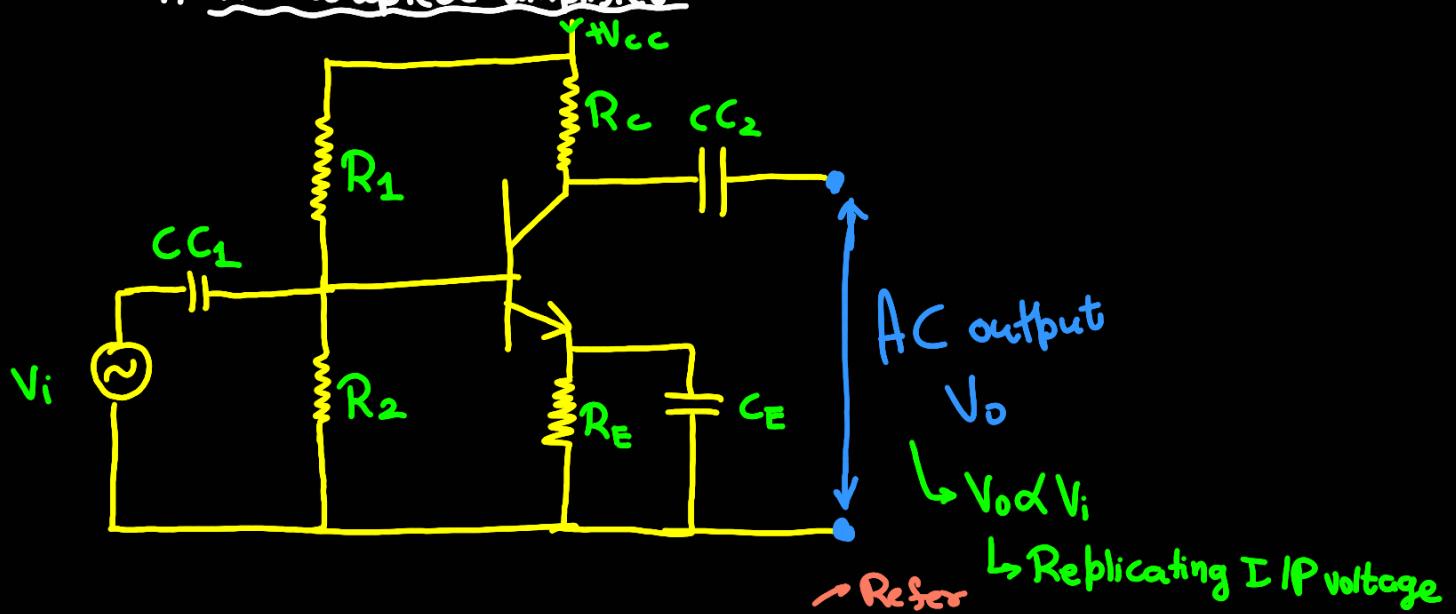

Functions:- ①  $R_C$  ②  $R_1 \& R_2$  ③  $R_E$  Bias method on top


④  $CC_1 \& CC_2$  :- Coupling capacitors; Blocks DC voltage and allow only AC voltage & improve AC gain

⑤  $C_E$  :- Bypass Capacitor acts as shunt across  $R_E$

$$\text{Voltage gain} = A_v = \frac{V_o}{V_i} \Rightarrow V_o = A_v V_i$$

∴ O/P voltage  $V_o$  is  $A_v$  times the input voltage  $V_i$


## \* Waveforms:-

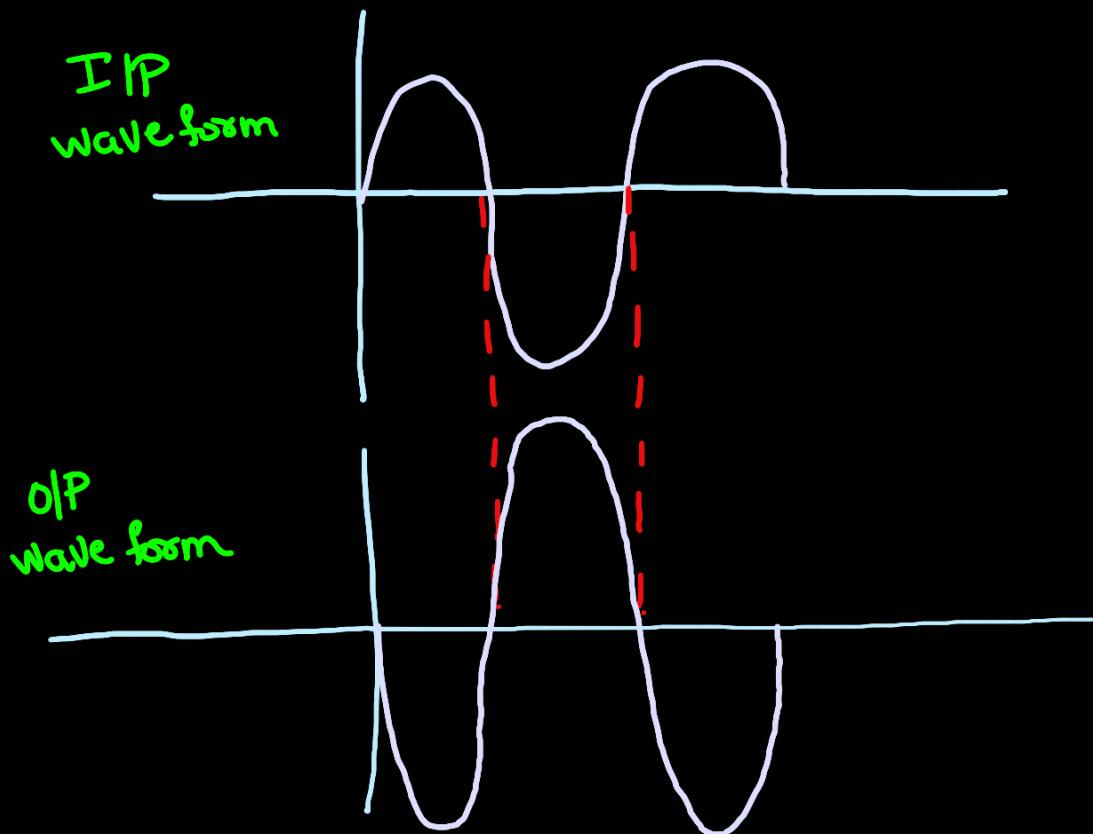

O/P is out of phase by  $180^\circ$

$$I/P \uparrow \Rightarrow O/P \downarrow$$

## \* Understanding frequency response:-

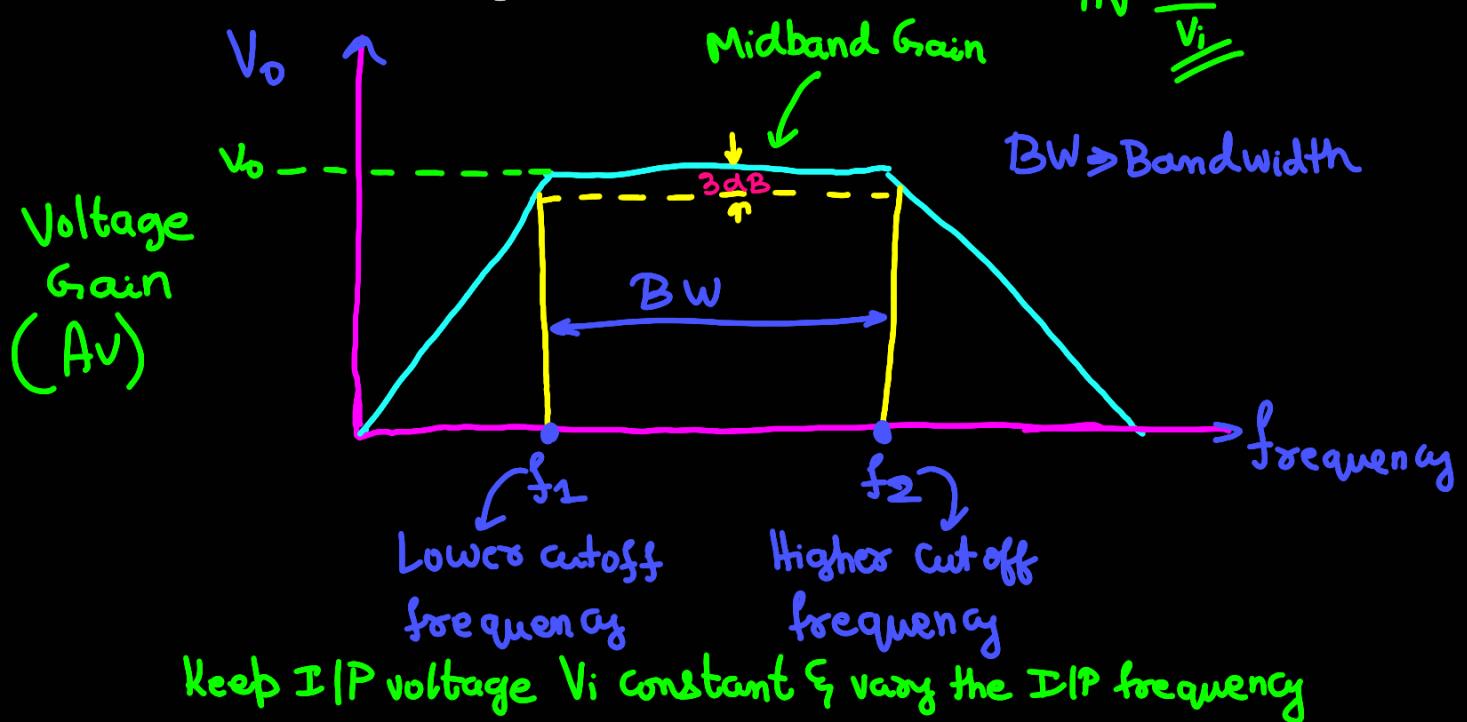

DC is blocked by capacitor. At 0 frequency, there is 0 O/P voltage.

$$X_C = \frac{1}{2\pi f C} \Rightarrow X_C \downarrow \Rightarrow f \uparrow$$

Increase in frequency, reactance reduces, O/P voltage increases

At one point it stabilizes at  $V_0$  for a certain frequency range called Bandwidth.

For a larger BW, we sacrifice gain and Vice-Versa

$$A_v(\text{dB}) = 20 \log_{10} \frac{V_o}{V_i} \text{ dB}$$

Voltage gain in dB


A.K.A midband gain

Gain Bandwidth Product = GBW

$\Rightarrow GBW = A_v \times BW$  } for a given amplifier, GBW is constant


## # Junction Field Effect Transistor (JFET) :-

Simply referred to as FET

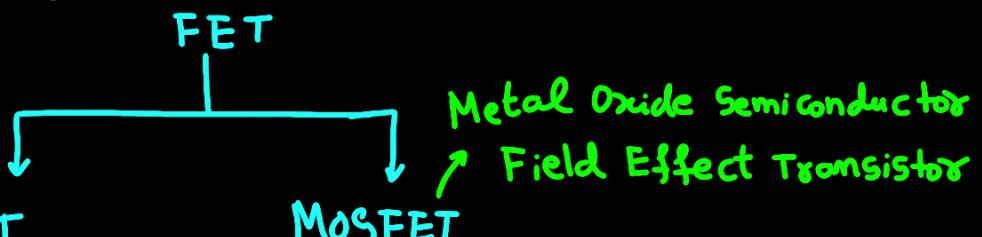

\* JFET: Consist of silicon semiconductor bar either N-type or P-type with opposite type of semiconductor material diffused on either side of the bar.

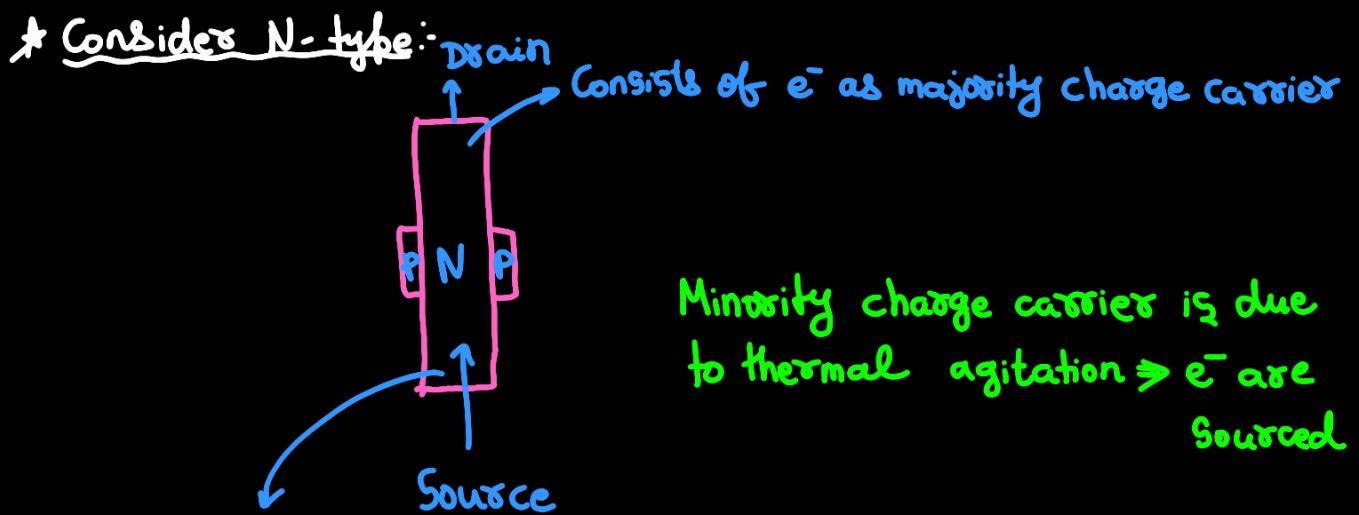i.e. → for N-type bar → P-type is diffused  
for P-type bar → N-type is diffused



Minority charge carrier is due to thermal agitation  $\Rightarrow e^-$  are sourced

$e^-$  move in one dir<sup>n</sup> based on biasing  
but always from -ve to +ve

Semiconductor bar consist of two terminals

\* Source  
\* Drain

P-type diffused to the bar forms a terminal called "gate"


$\therefore$  JFET is a three terminal device consisting of source, drain & gate

$e^-$  move from source to drain when proper voltage is applied b/w source & drain.


$\downarrow$                $\downarrow$   
 -ve              +ve  
 Voltage      Voltage

\* JFET is either N-channel or P-channel  
(The bar is the channel)

## # Circuit symbol for JFET:-

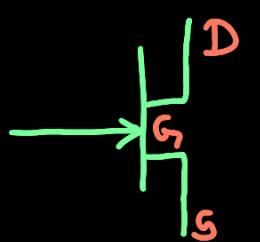

N-channel FET

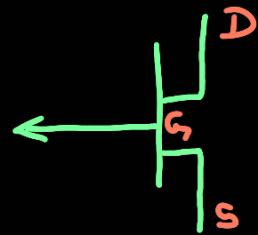


P-channel FET

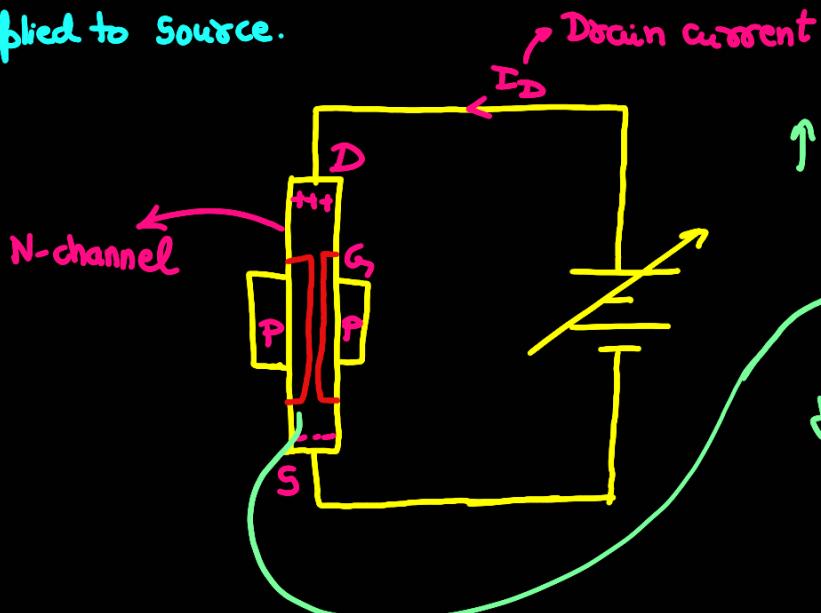
## # Characteristics of JFET:-

→ O/P characteristics

Consider N-channel FET, +ve voltage applied to drain, -ve voltage applied to Source.



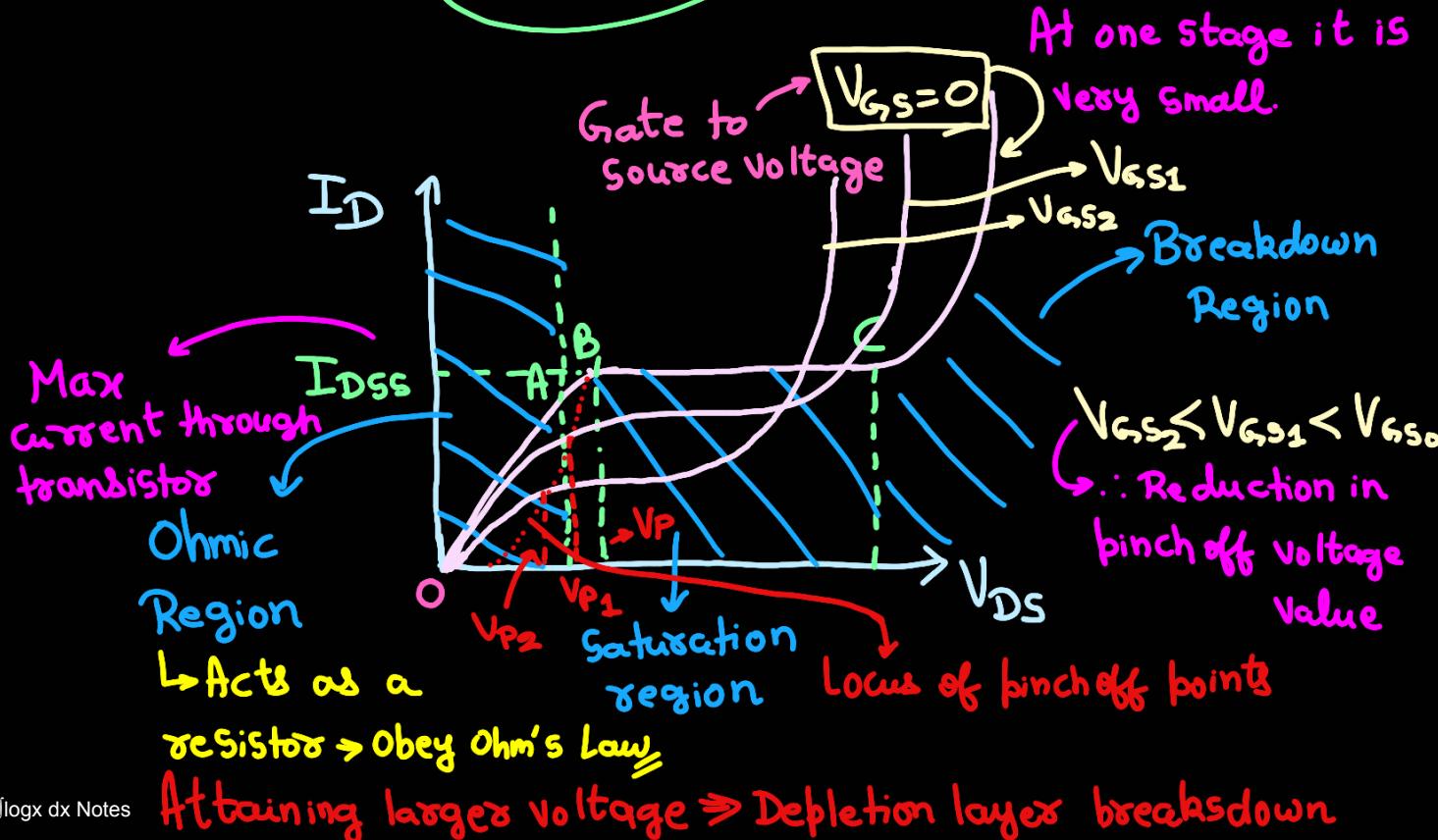$\uparrow e^-$  in voltage  $\rightarrow$  more  $e^-$  near Drain  
 Depletion region formed penetrates through channel  $\downarrow$   
 (conducting path reduces)




→ O to A → Ohmic Region

→ A to B → Drain keeps decreasing because of depletion region b/w gate & drain

→ At B, drain current is pinched off.

Point B is called Pinchoff point

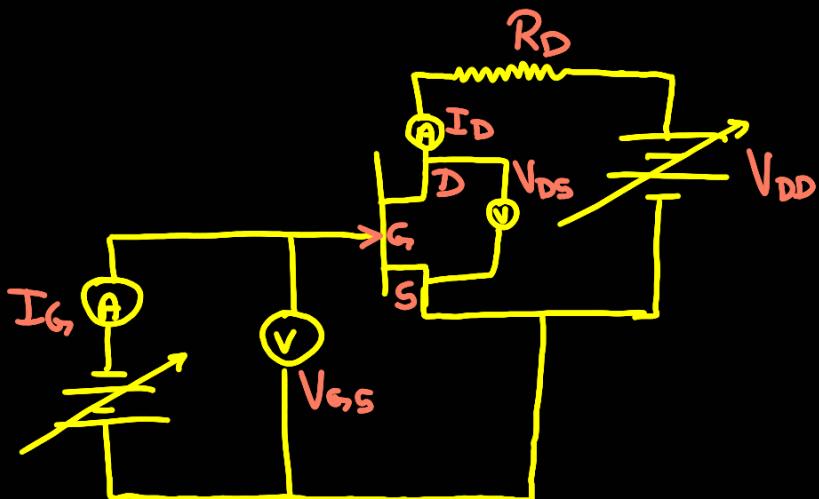The drain to source to source voltage ( $V_{DS}$ ) at B is Pinchoff Voltage



Therefore, there is no I/V characteristics

$I_G = 0$  as P-N junction here is operated in reverse bias  
Only a very small negligible saturation current flows which is  $\approx 0$

$\mu = \frac{\Delta V_{DS}}{\Delta V_{GS}}$  → Amplification factor

# Transfer characteristics of JFET:-

Remember!!

$$V_P = V_{GS0}$$

$V_P$

$-V_{GS}$

$I_D$   
 $I_{DSS}$

$I_{D1}$

Operating points

$V_{GS}$

\* O/P resistance =  $\gamma_d = \frac{\Delta V_{DS}}{\Delta I_D}$   
 (From O/P char)

\* Transconductance ( $g_m$ ) =  $\frac{I_D}{V_{GS}}$

\* Transconductance ( $g_m$ ) =  $\frac{\Delta I_D}{\Delta V_{GS}}$

$$\begin{aligned} \therefore \mu &= \frac{\Delta V_{DS} \times I_D}{\Delta V_{GS} \quad I_D} \\ &= \frac{\Delta V_{DS} \times \Delta I_D}{\Delta I_D \quad \Delta V_{GS}} \\ &\downarrow \quad \downarrow \\ \gamma_d & \quad g_m \end{aligned}$$

$\therefore \mu = \gamma_d \cdot g_m$



## # Current Equation of JFET:-

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

To remember

$$\begin{aligned} V_{DS} &= V_{DD} - I_D(R_s + R_D) \\ V_{GS} &= -V_S = I_S R_S = I_D R_S \\ V_{DS} &= V_D - V_S \end{aligned}$$


## # Difference b/w BJT & JFET:-

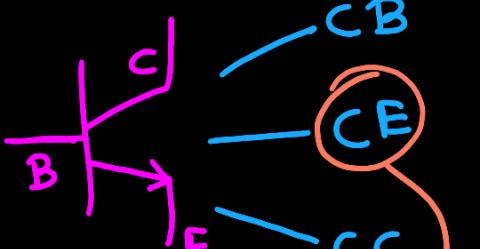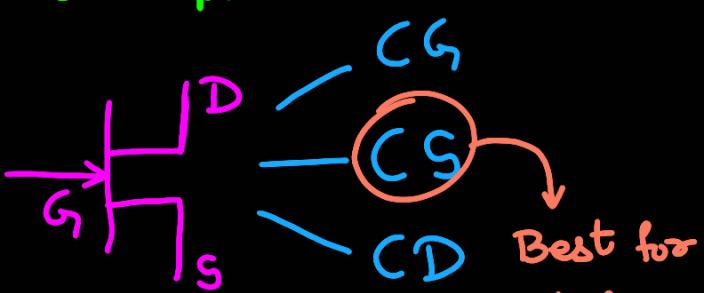BJT	FET
* Current operated device	* Voltage operated Device
* Both majority & minority carriers are used for conduction Thus "Bipolar"	* Only majority carriers are used for conduction Thus "Unipolar"
 Best for amplifiers	 Best for amplifiers

## # CS amplifier:-

Common Source amplifier

↳ Gate to Source Reverse Bias

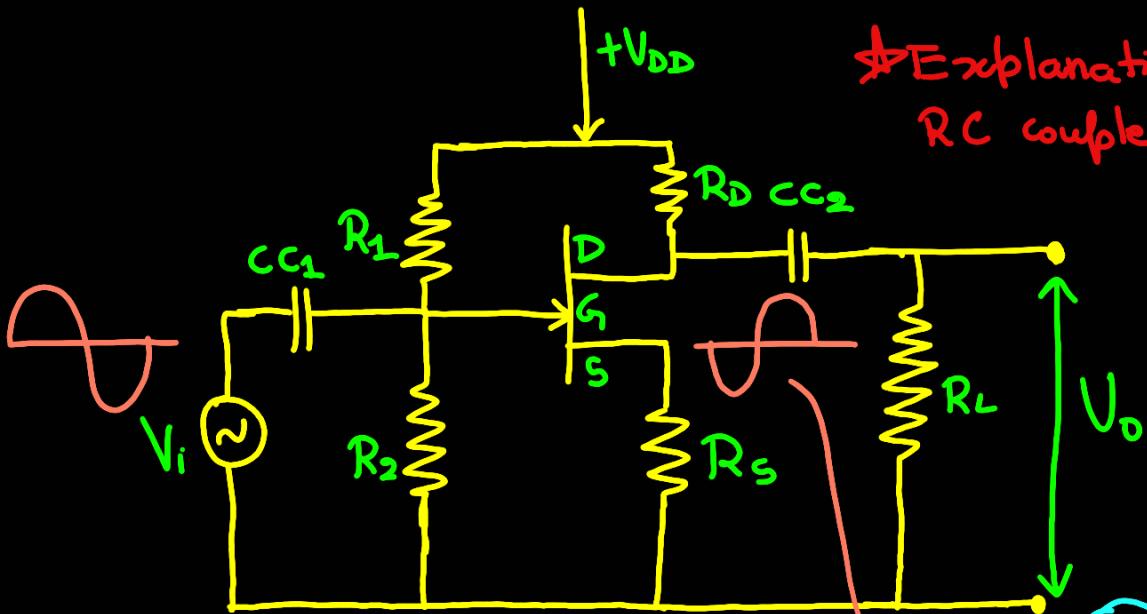

\*Explanation Same as RC coupled CF

$$I_D = I_S$$


Phase shift b/w I/P & O/P voltage is  $180^\circ$

$$V_{DD} = I_D R_D + V_{DS} + I_S R_S$$

$$\Rightarrow V_{DD} = V_{DS} + I_D (R_D + R_S)$$



$$\therefore \mu = \frac{\Delta V_{DS}}{\Delta V_{GS}} \Rightarrow V_{DS} = \mu V_{GS}$$

\*Understanding frequency response:-

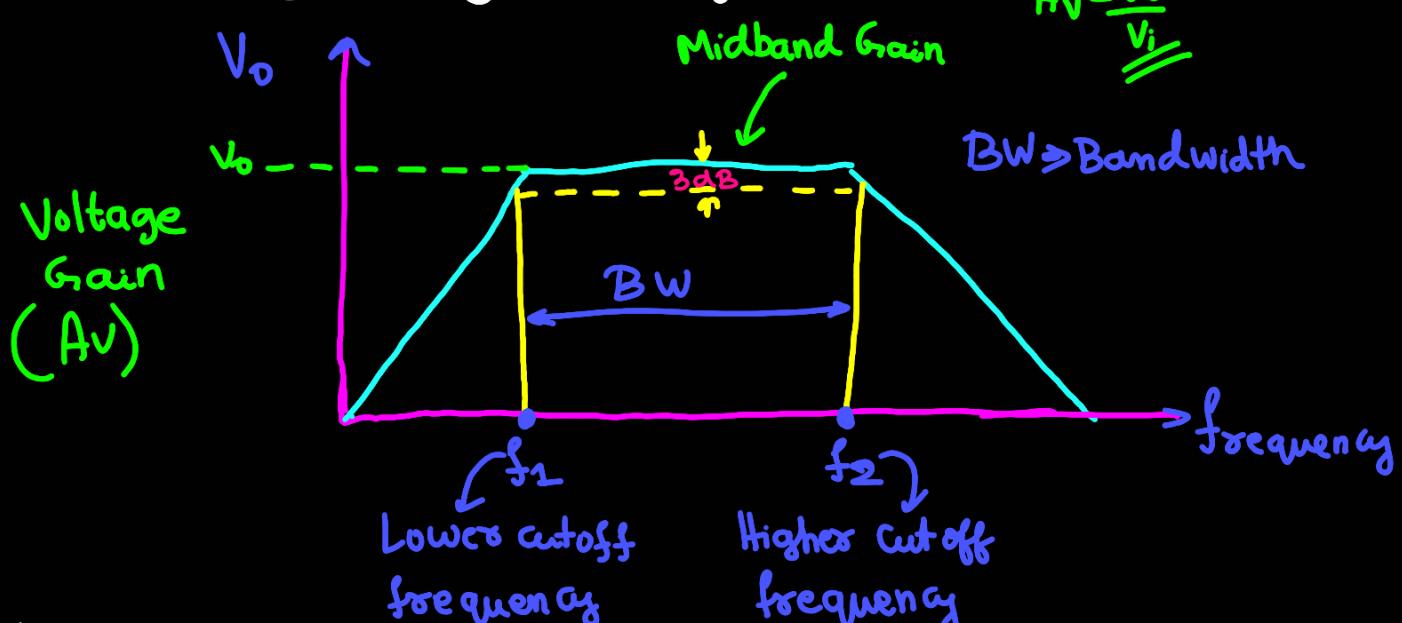

Keep I/P voltage  $V_i$  constant & vary the I/P frequency


## # DC analysis:-

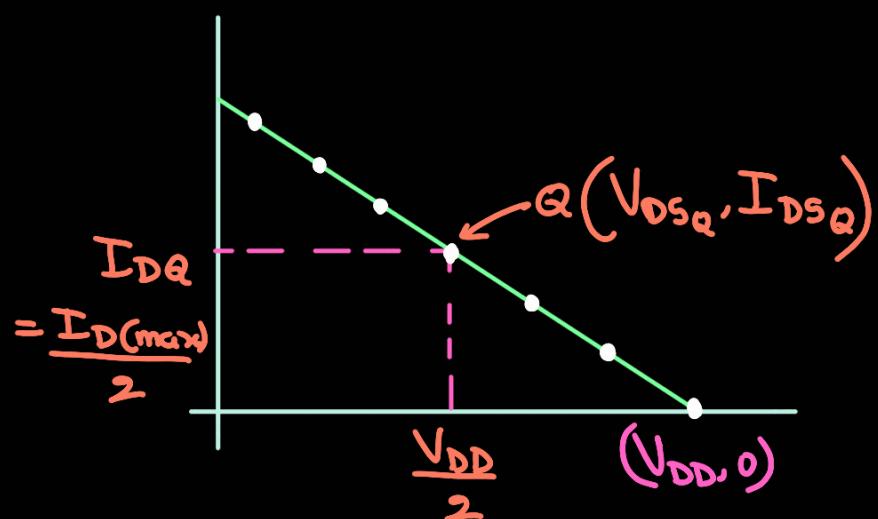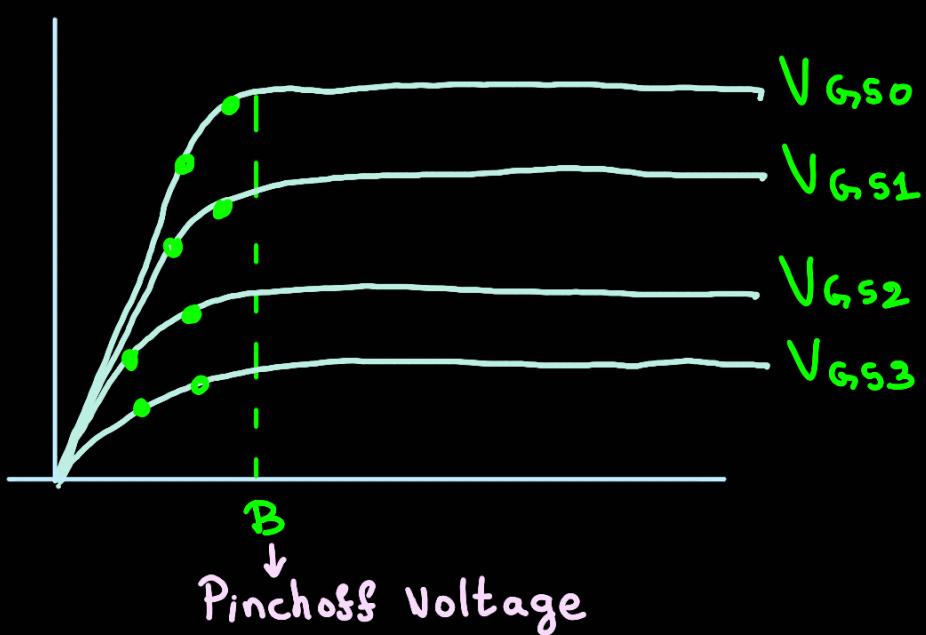

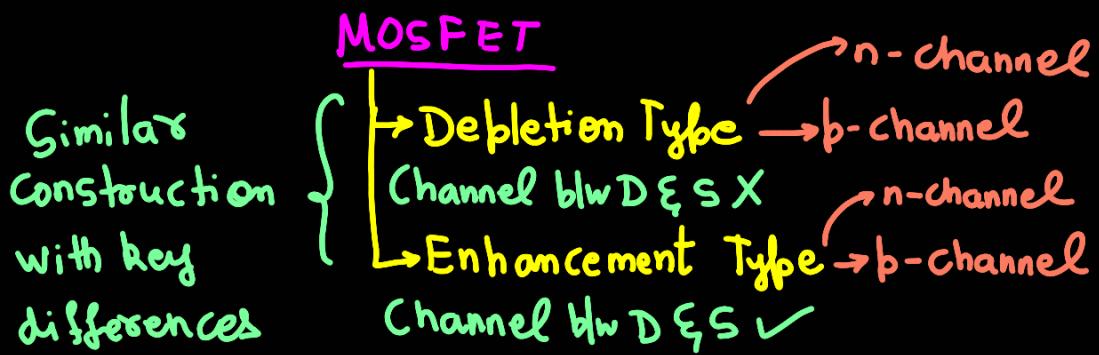
## # MosFET:-

↳ Metal Oxide Semiconductor Field Effect Transistor


Active Device → Ability to control the flow of e<sup>-</sup>s


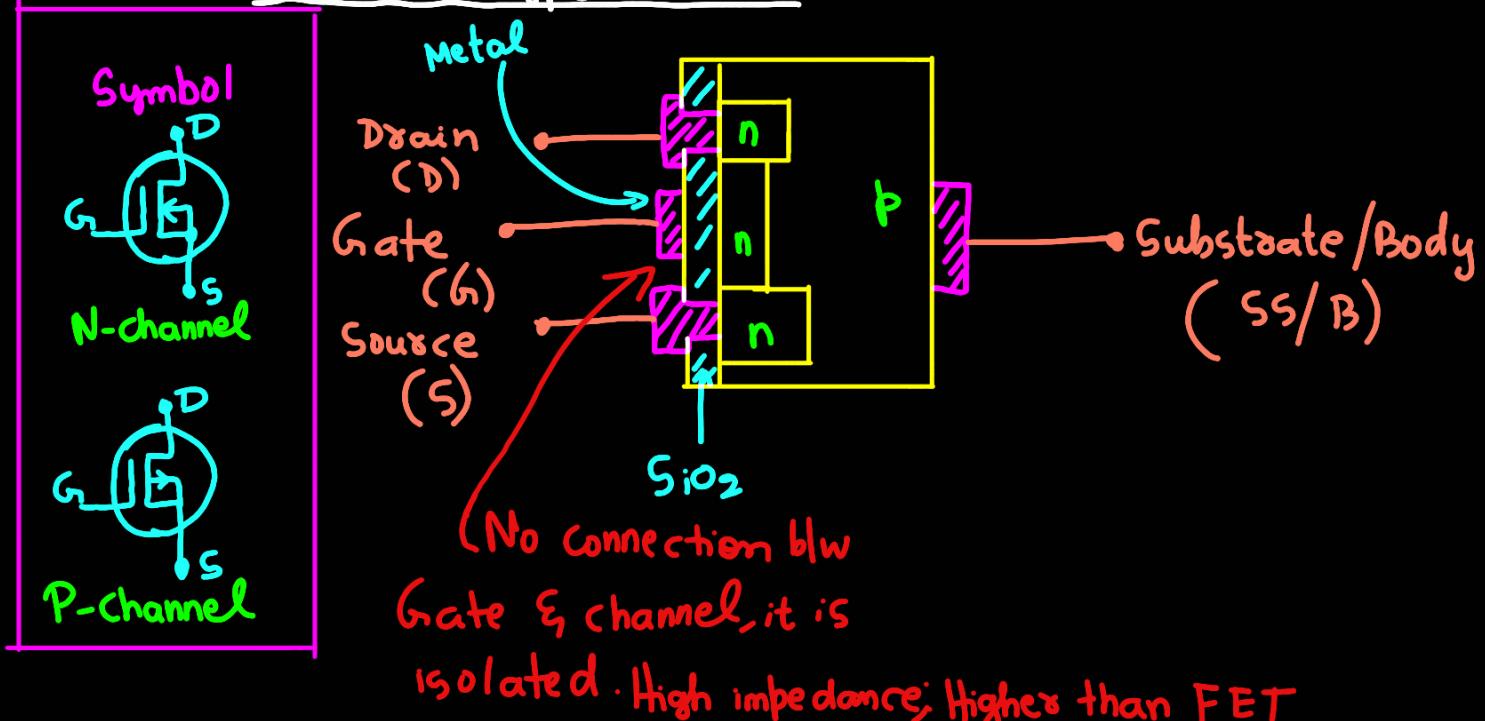
## # Depletion Type MOSFET:- Consider N-channel




## # Working of Depletion Type MOSFET:-

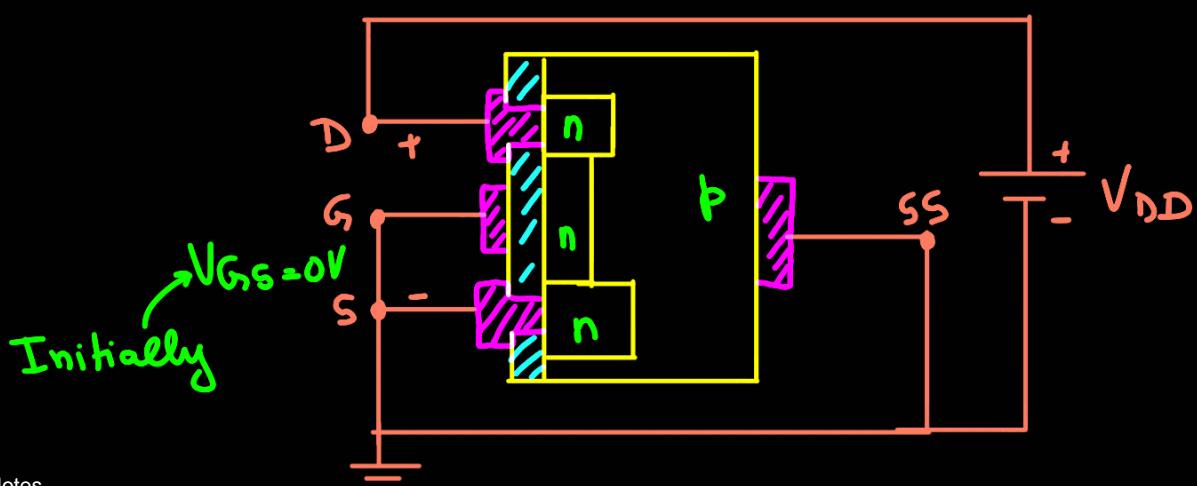



$e^-$  in n-channel get attracted to +ve terminal

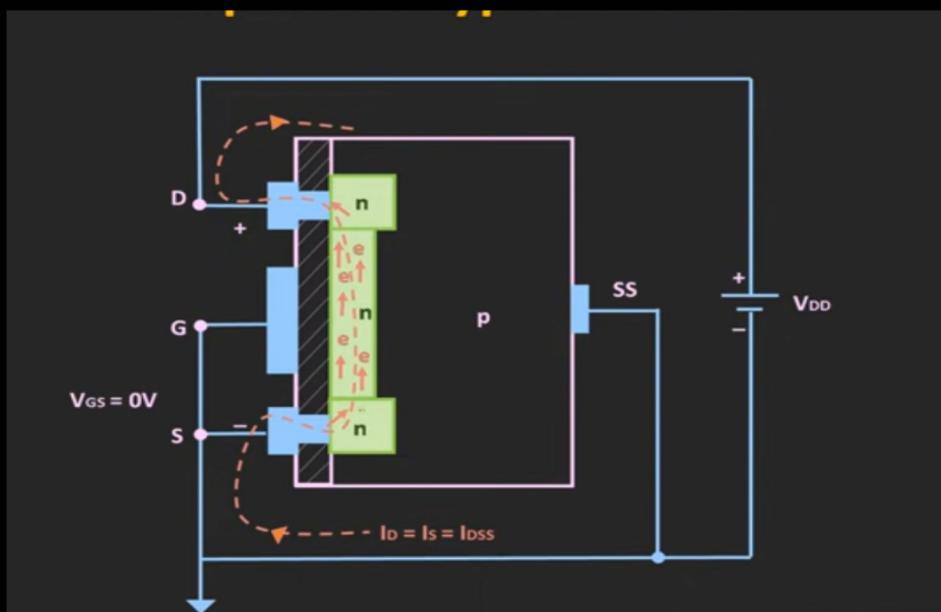This process continues until all  $e^-$  have contributed to flow of current




Later on ↑ Voltage, Current will be constant


### \* Drain/O/P characteristics:-

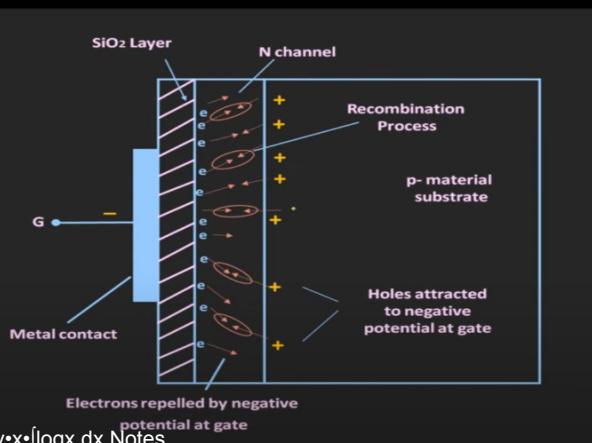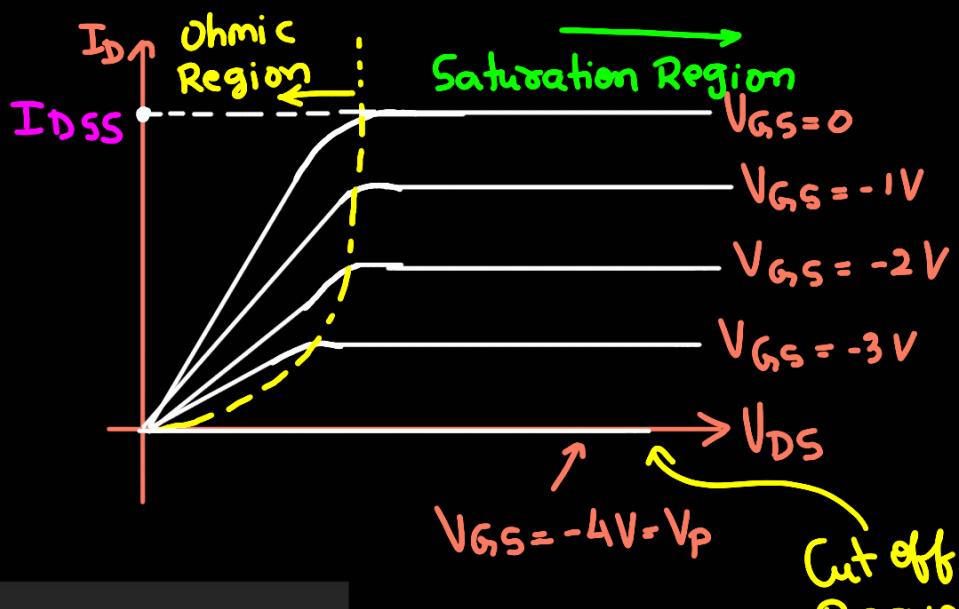


Application of -ve Voltage

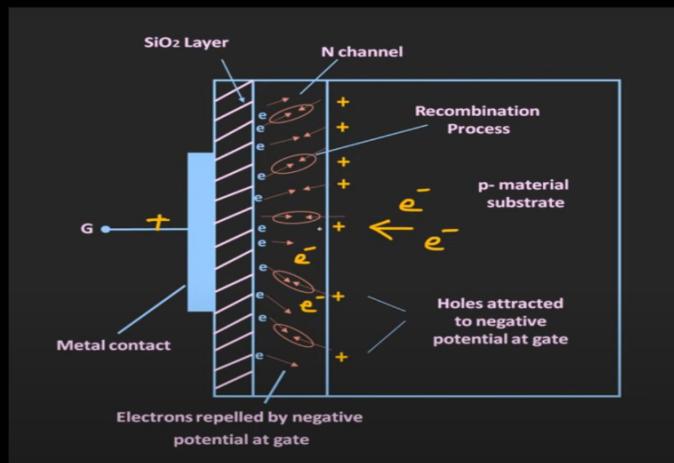

Application of +ve voltage

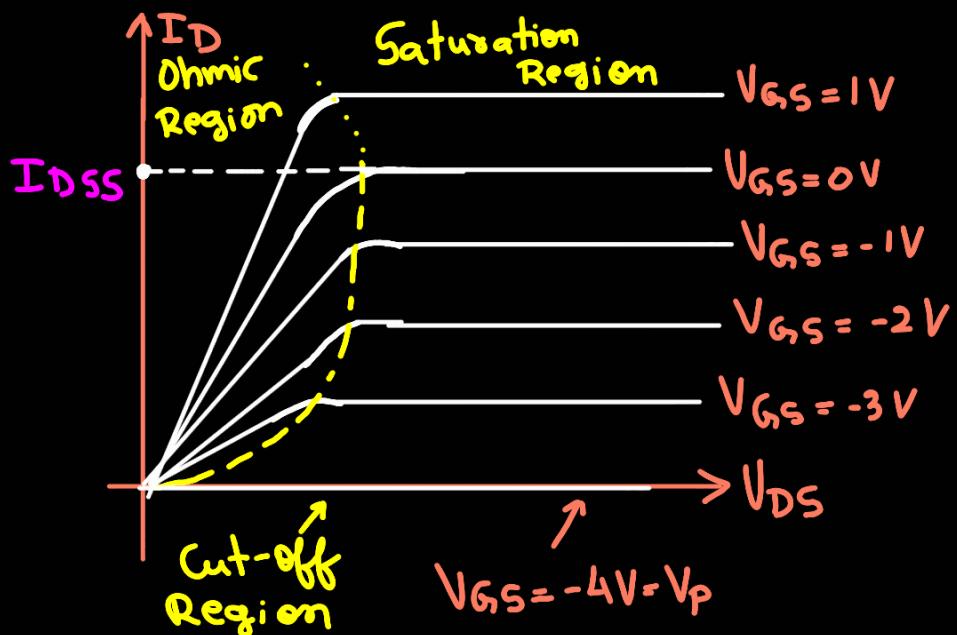




\* Transfer characteristics :-

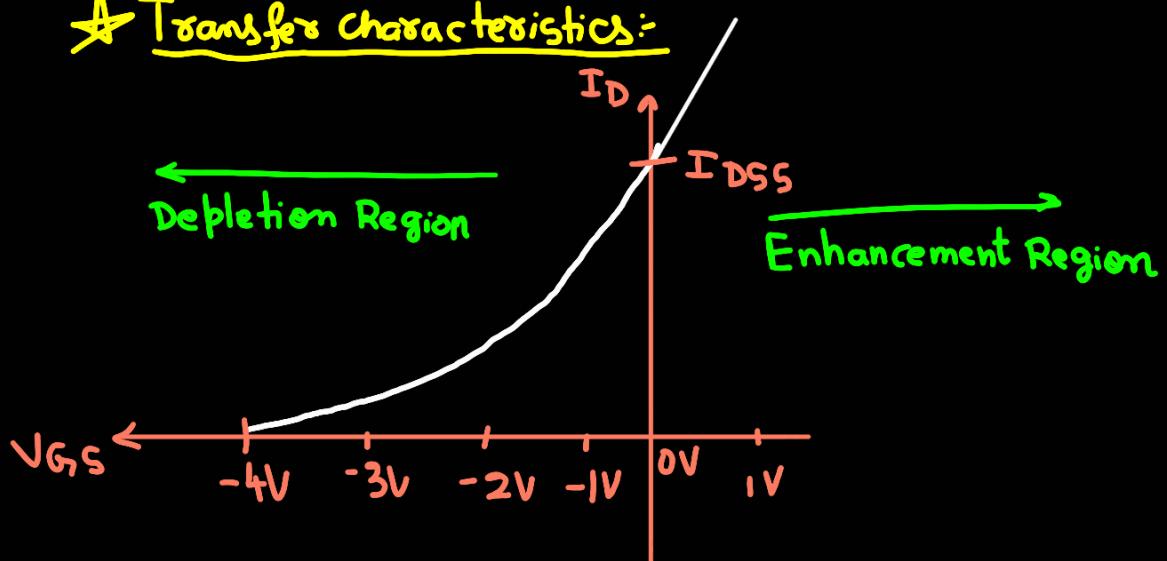


$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$

Eq<sup>n</sup> for Depletion type MOSFET.  
Same as JFET

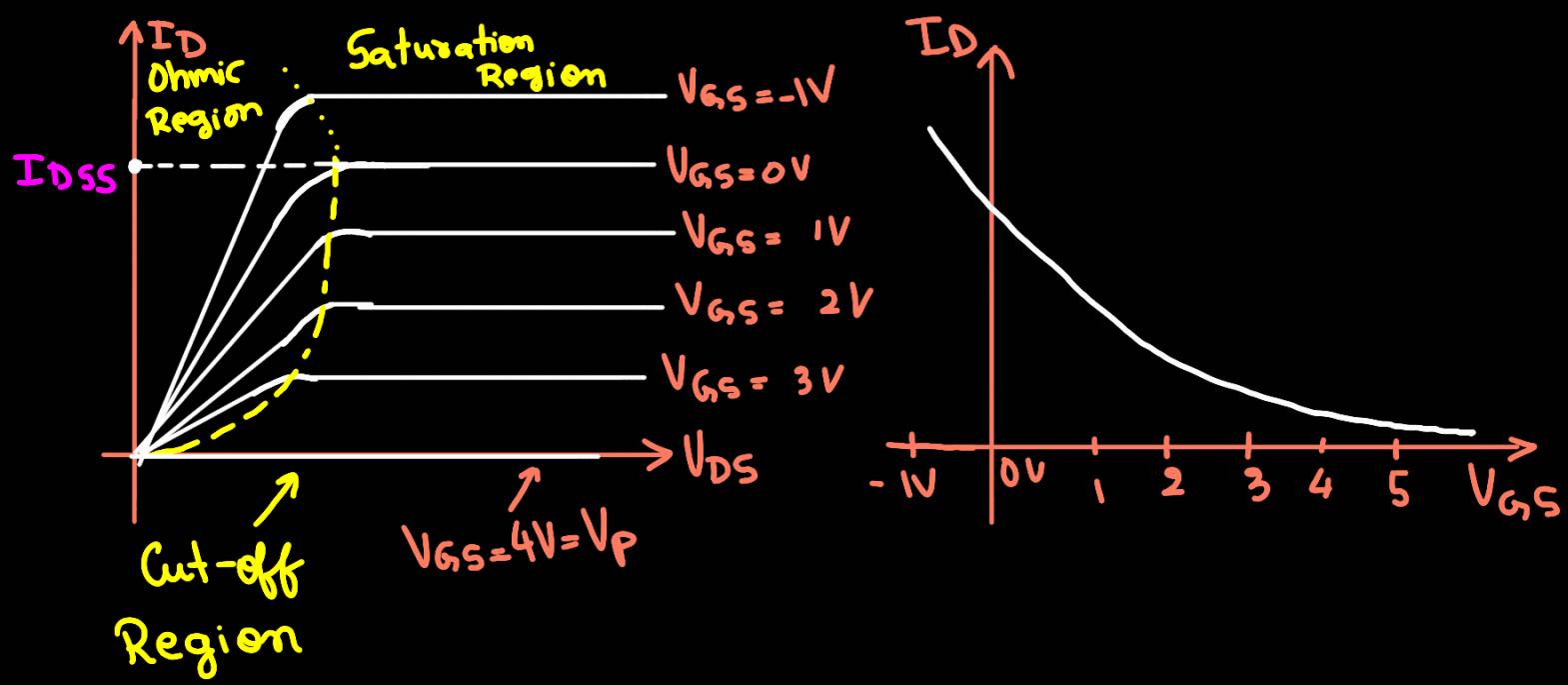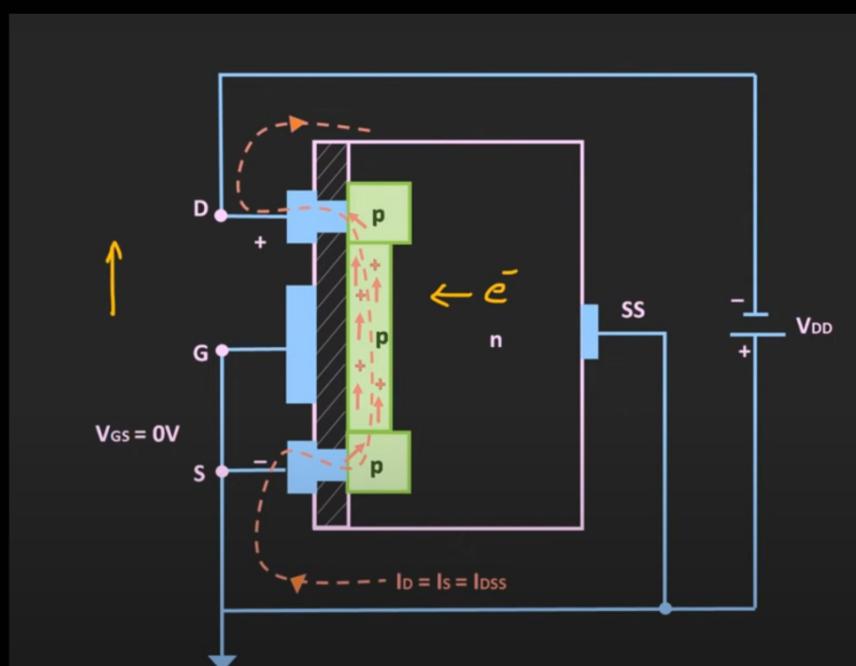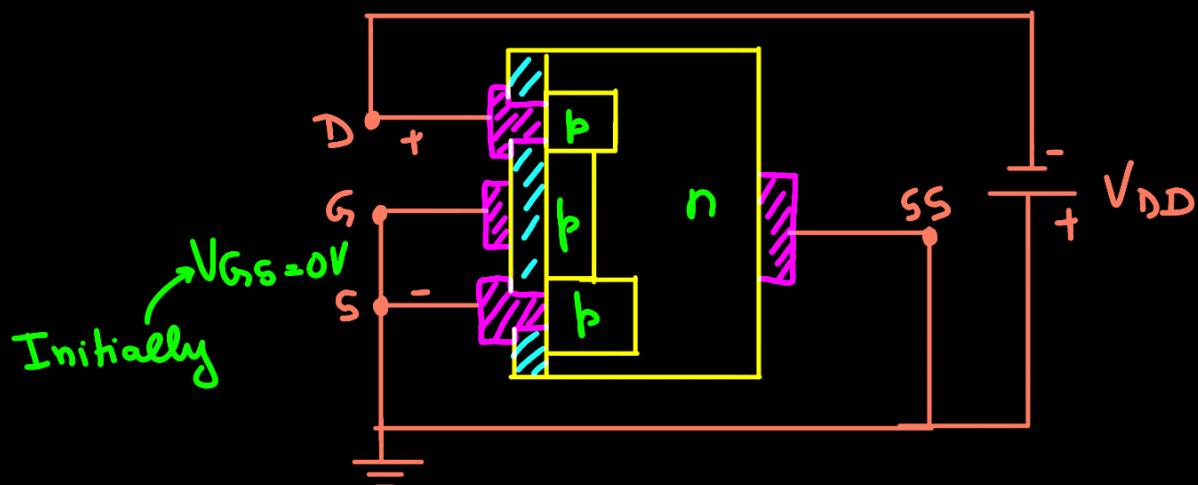
# \* Depletion type P-channel MOSFET Same as N-channel but polarity reversed




## # Enhancement type MOSFET:-

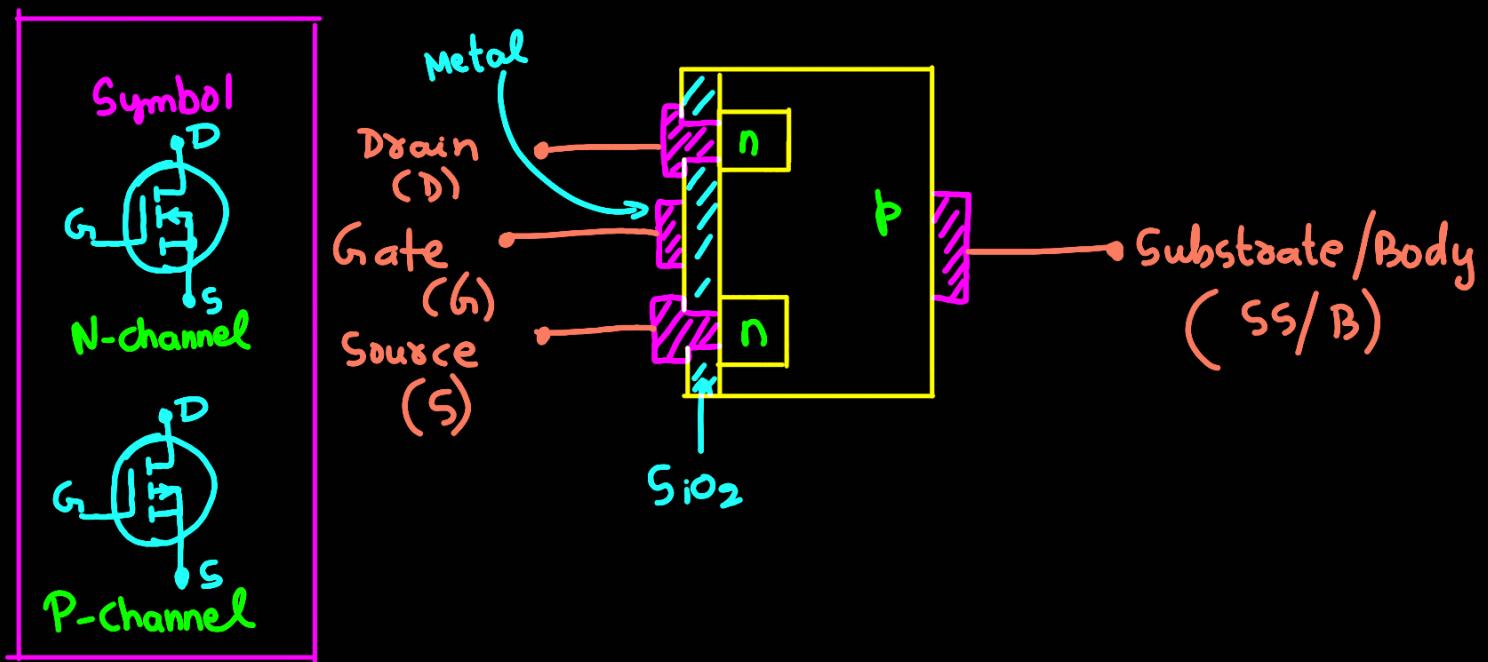


**Threshold Voltage ( $V_{th}$ ):** The key feature of an enhancement MOSFET is the threshold voltage. For an N-channel MOSFET, when the gate-to-source voltage ( $V_{GS}$ ) is greater than the threshold voltage ( $V_{th}$ ), a conductive channel forms between the drain and source, allowing current to flow. For a P-channel MOSFET, the gate-to-source voltage needs to be less than the threshold voltage to turn on the device.

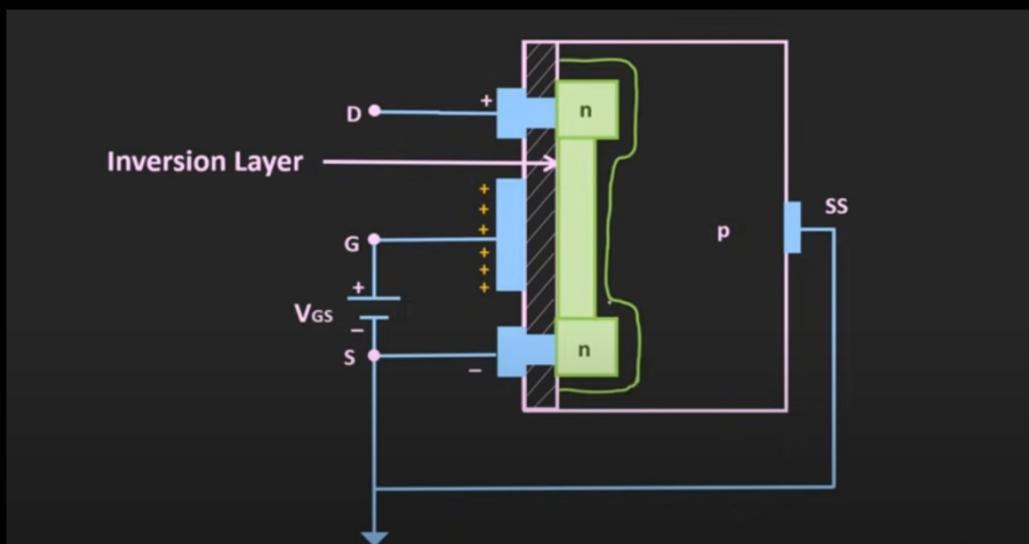

## ★ Drain Characteristics

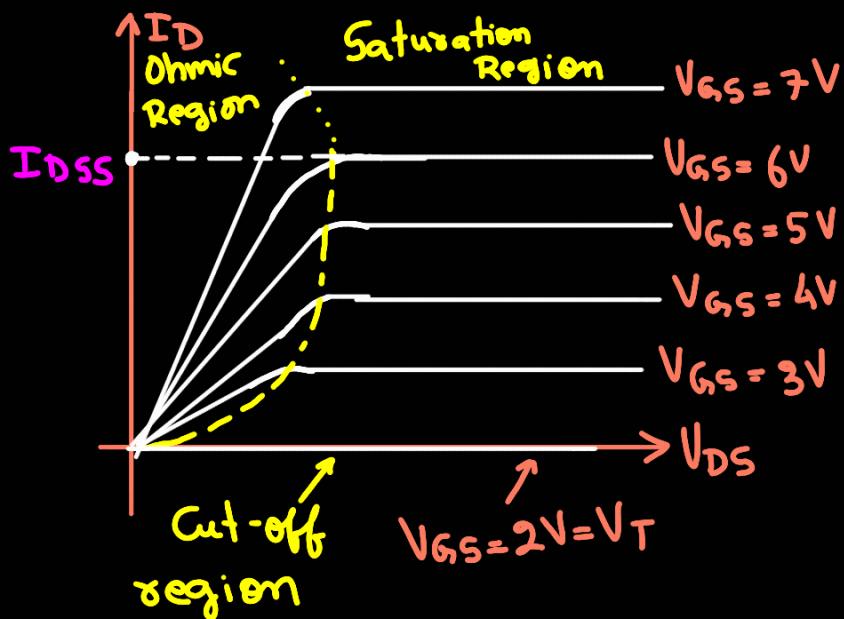

## ★ Transfer Characteristics

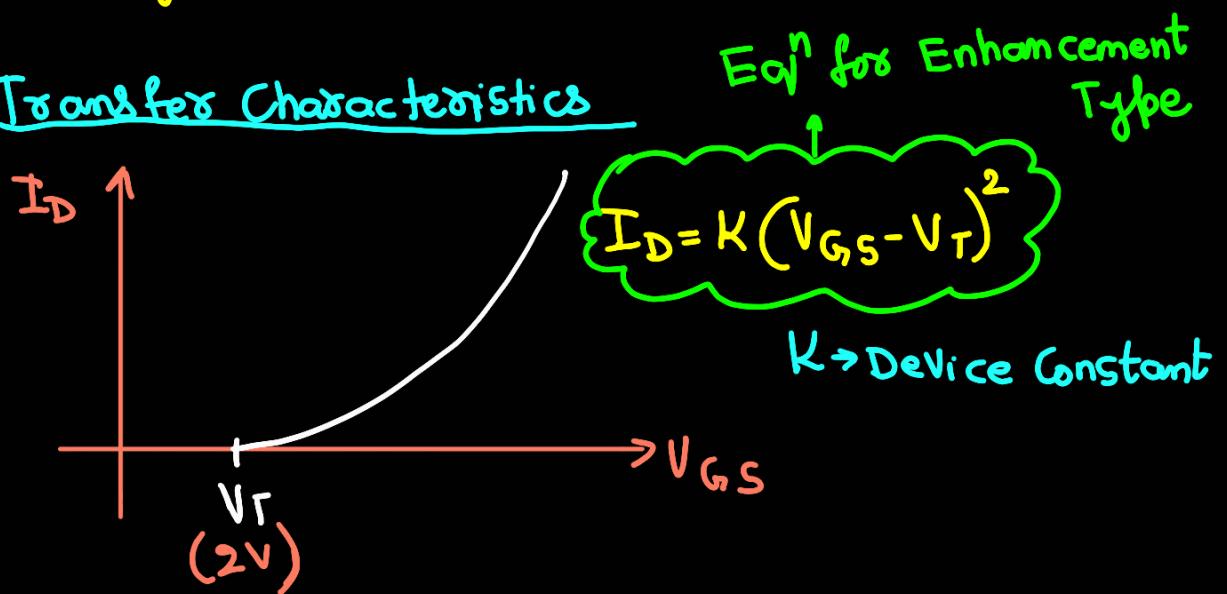

P Channel MOSFET is Similar

Just Change the Polarity



OR

Refer below notes for  
MOSFETS

transfer conductance =  $\frac{\Delta I_D}{\Delta V_{DS}}$  =  $g_m$

output impedance,  $R_o = \frac{\Delta V_{OS}}{\Delta I_D}$  ||  $V_{DS}$

amplification factor:

$A = \frac{O/P \text{ Voltage}}{I/P \text{ Voltage}}$

$A = \frac{V_{DS} \times I_D}{V_{GS} \times I_D}$

$$= \left( \frac{V_D}{I_D} \right) \left( \frac{I_D}{I_{DS}} \right)$$

$$= \left( \frac{\Delta V_D}{\Delta I_D} \right) \left( \frac{\Delta I_D}{\Delta V_{DS}} \right)$$

$$A = k \cdot g_m$$

### (a) MOSFET [Metal-oxide semiconductor field effect T.]

\* It is unipolar device operating on  $N$  channel.

\* Operates on voltage.

\* Insulator separates the gate from channel.

\* There are two MOSFETs they are  $N$  type.

$\Rightarrow$  Depletion type MOSFET.


\* In this MOSFET the channel is made up of  $N$ -type of material & the substrate is of  $P$ -type of material.

\*  $SiO_2$  is the metallic contact which separates the gate & the channel.


\* Gate terminal is isolated from the channel due to the  $SiO_2$  layer & partial channel setup below  $SiO_2$ .



### Symbol

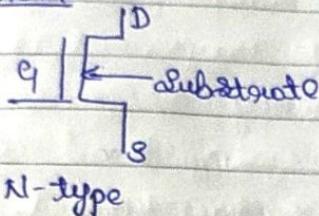


N-type

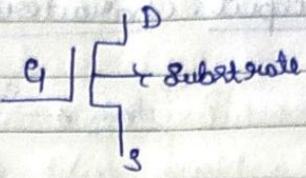

P-type

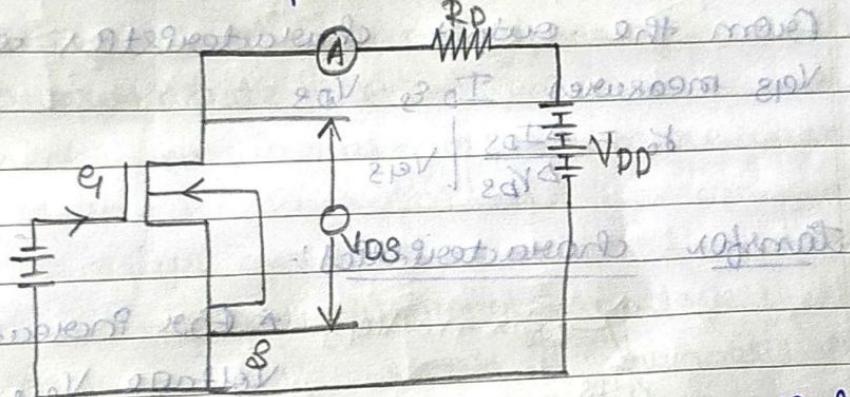- \* Due to this insulator input impedance of the gate terminal is very high. Hence MOSFET used in the application where minimum power consumption is required.



- \* When  $V_{GS} = 0$  & +ve voltage is applied b/w D & S terminal towards the one side of insulator, the other side it induces the -ve charge.

- \* Hence the electron in the N-channel increases results in increase in the  $I_D$ .

- \* The value of the saturation current for  $V_{GS} = 0$  is called  $I_{DS}$ .

- \* If the  $V_{GS} = 0$  the point is called pinch-off voltage.


- \* The voltage at which  $V_{GS} = V_p$  is called cut-off region.

- \* The depletion curve also works for the +ve voltage on which  $I_D$  increases.



REDMI NOTE 8  
AI QUAD CAMERA


### Output characteristics:

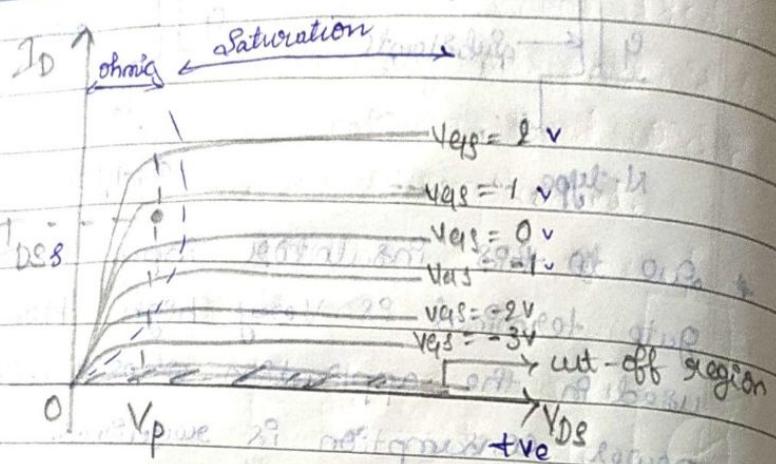

From the output characteristics at given  $V_{GS}$  measures  $I_D$  &  $V_{DS}$

$$g_o = \frac{\Delta I_D}{\Delta V_{DS}} \Big|_{V_{GS}}$$

### Transfer characteristics:

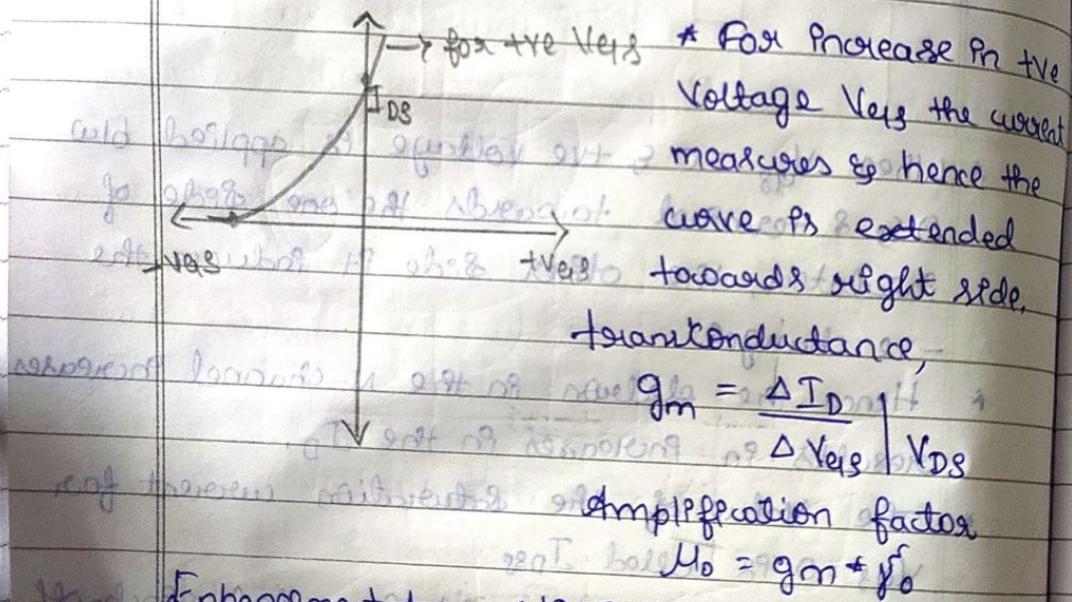

transconductance,

$$g_m = \frac{\Delta I_D}{\Delta V_{GS} | V_{DS}}$$


amplification factor

$$20T \cdot 10^3 M_0 = g_m \cdot g_f$$
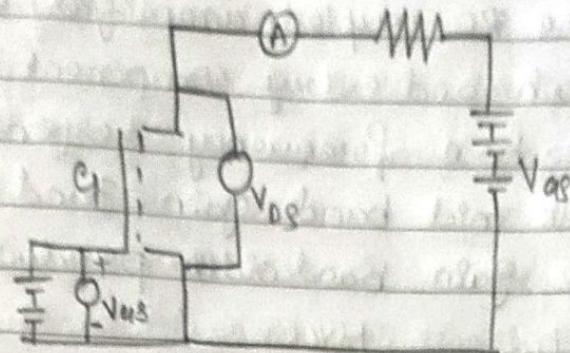
### Enhancement type MOSFET:


- Substrate is made up of p-type semiconductor
- $\text{SiO}_2$  isolates the gate terminal & p-substrate
- there is no channel b/w drain & source
- When the controlled voltage is applied b/w drain & source then channel is formed.





- \* When  $V_{GS} = 0$  the voltage is applied b/w D & S then current flows in MOSFET
- \* When +ve voltage applied b/w G & S then holes near the G pushed away & e- attracted towards gate terminal.
- \* When  $V_{GS}$  increases more & more channel is created.
- \* The value of  $V_{GS}$  at which the current increases is called threshold voltage.
- \* When  $V_{GS} > V_{TH}$  width of channel will increase.
- \* The voltage  $V_{DS}$  at which the pinch-off condition occurs is called saturation voltage.

### Output characteristics

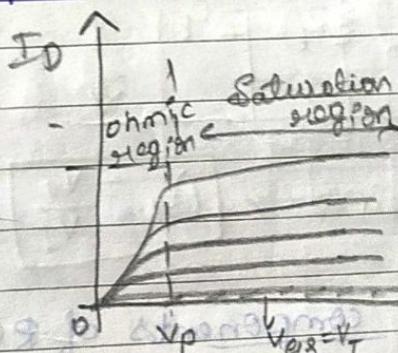

$$k_o^f = \frac{\Delta I_D}{\Delta V_{DS}} \Big|_{V_{DS}}$$

transfer C. :-



current decreases as VGS is increased

$$T_{DS} = k \times (V_{GS} - V_T)^2$$

REDMI NOTE 6D  
AI QUAD CAMERA

# Difference between JFET, BJT & MOSFET

Feature	JFET	MOSFET	BJT
<b>Control Mechanism</b>	Voltage applied to gate controls current	Voltage applied to gate controls current	Current applied to base controls current
<b>Gate Structure</b>	Junction gate	Metal-Oxide-Semiconductor gate	Base (with junctions)
<b>Input Impedance</b>	High	Very high	Low to moderate
<b>Switching Speed</b>	Faster than BJT	Very fast (faster than JFET)	Slower compared to FETs
<b>Power Consumption</b>	Low	Low	Higher due to base current
<b>Thermal Stability</b>	Good	Excellent	Poor
<b>Current Type</b>	Unipolar (one type of carrier)	Unipolar (one type of carrier)	Bipolar (both types of carriers)
<b>Ideal Amplifier Configuration</b>	Common Source	Common Source or Common Drain	Common Emitter